

# CSE 31

# Computer Organization

Lecture 24 – CPU Design (3)


# Announcement

- ▶ No lab this week
  - Project #1/2 grading during lab
- ▶ HW #7 at zyBooks
  - Due Monday(12/10) at 11:59pm
- ▶ Project #2
  - Due Monday (12/3)
    - Don't start late, you won't have time!
- ▶ Course evaluation online
  - Fill out by 12/6 (Thursday)
- ▶ Reading assignment
  - Chapter 5.7 – 5.11 of zyBooks (Reading Assignment #6)
    - Make sure to do the Participation Activities
    - Due Wednesday (12/5)


# Announcement

- ▶ zyBooks assignment Re-dos
  - Re-submit at most 5 reading assignments or HW (zyBooks only)
  - Email to me (not your TAs)
    - Include your name, assignment numbers
    - (Monday) 12/10 at 11:59pm, no extension
  - Fill out online evaluation by 12/6, tomorrow (70% of class)
- ▶ Final Exam
  - 12/11 (Tuesday), 11:30 – 2:30pm
  - Cover all
  - Practice exam in CatCourses
  - Closed book
  - 2 sheet of note (8.5" x 11")
  - MIPS reference sheet will be provided
  - Review: 12/10 (Monday) 1-3pm, COB 113

# Single Cycle Datapath

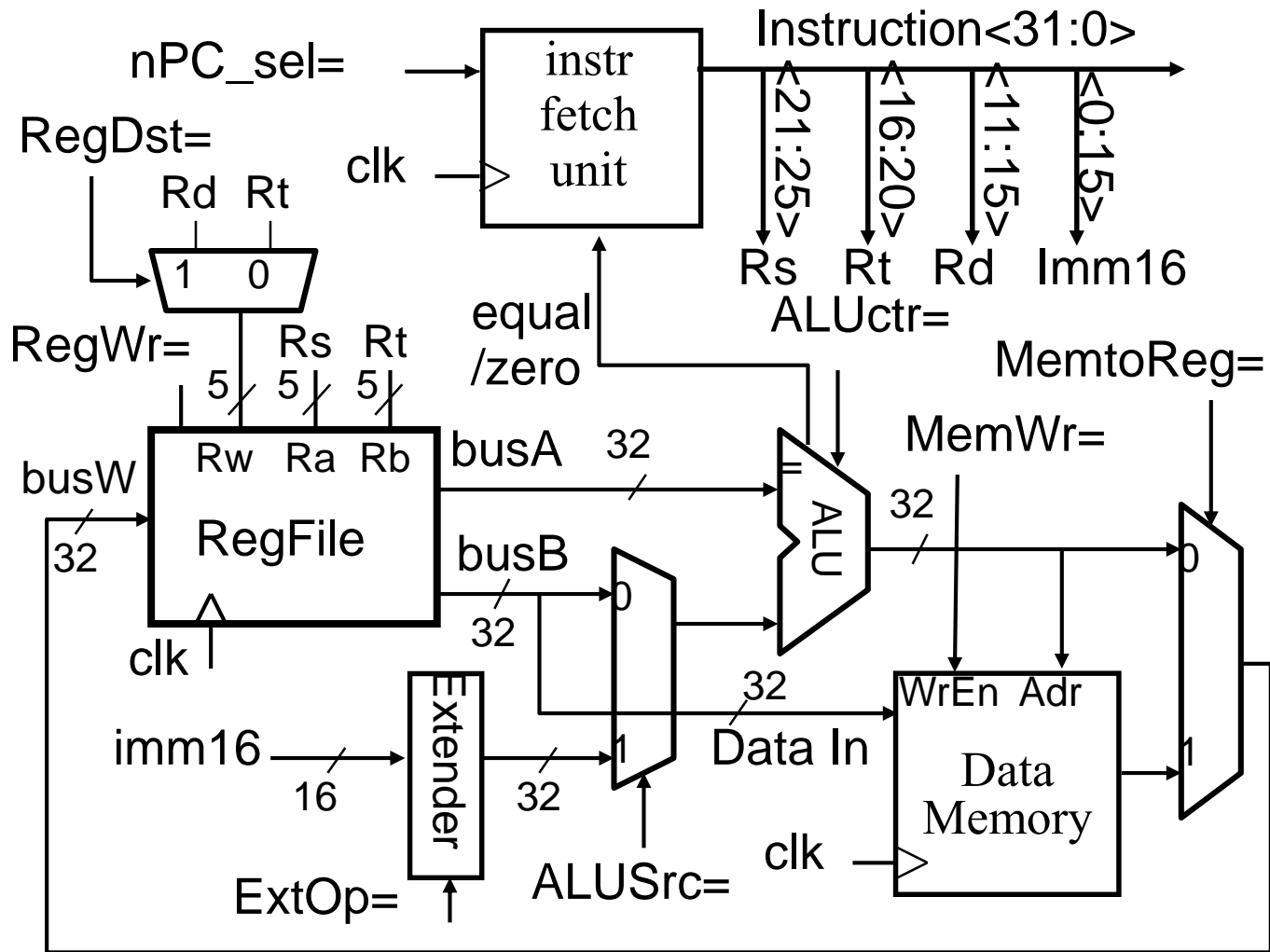

# The Add Instruction

 

add rd, rs, rt


- MEM[PC]                      Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$       The actual operation
- $PC = PC + 4$  Calculate the next instruction's address

# Instruction Fetch Unit start of Add


- Fetch the instruction from Instruction memory:

Instruction = MEM[PC]


- same for all instructions

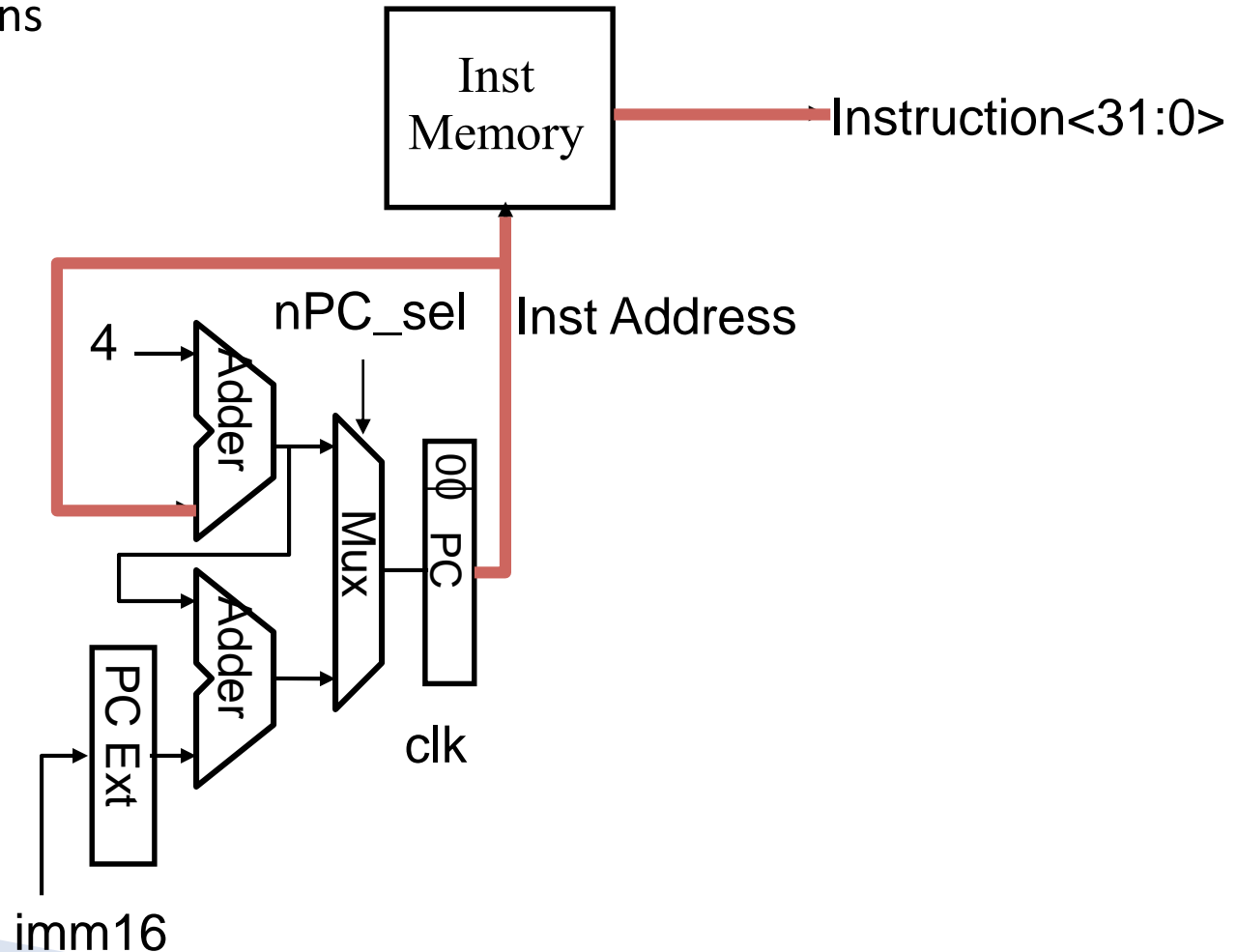

# The Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

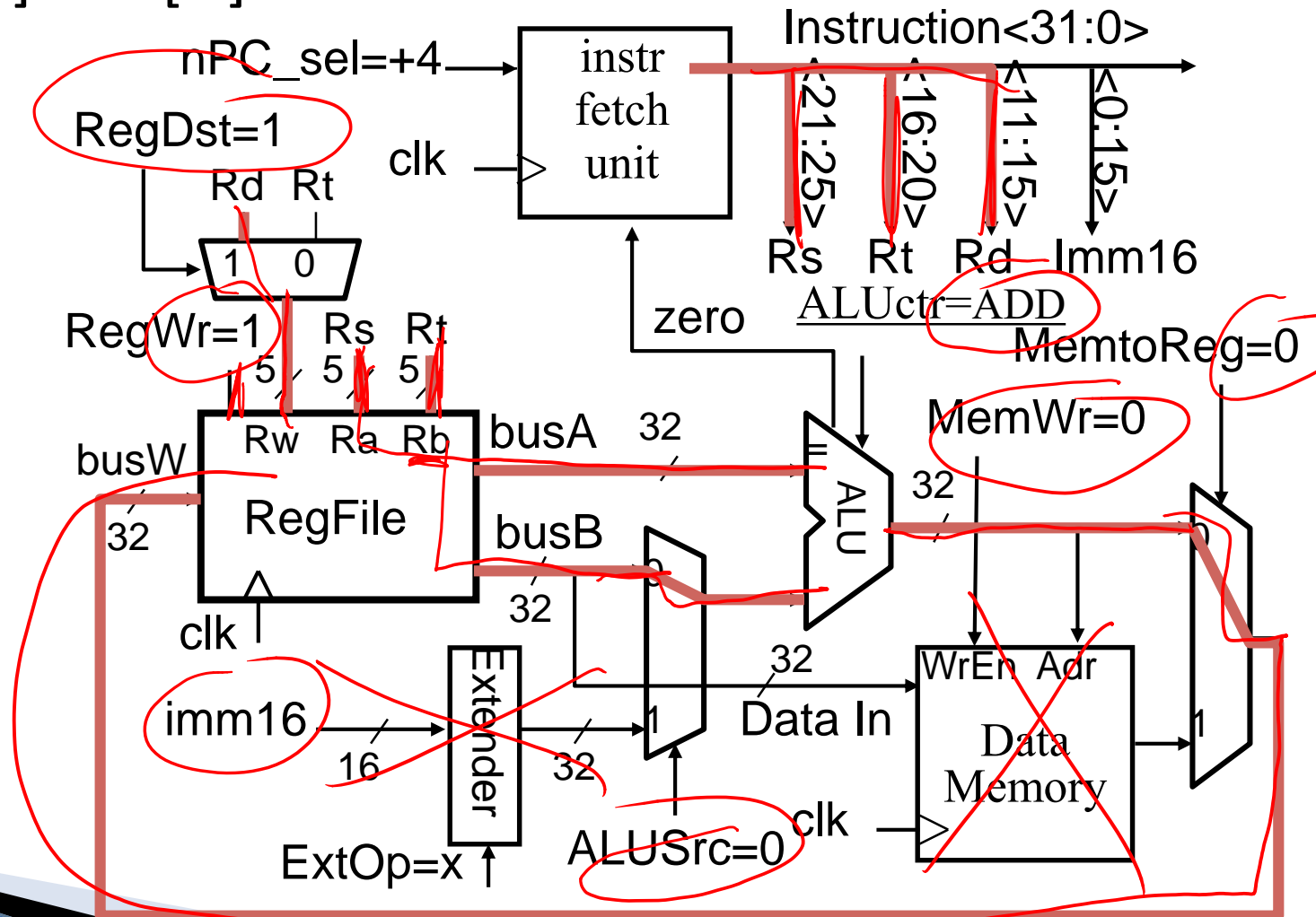
 
# Instruction Fetch Unit end of Add


►  $PC = PC + 4$

- This is the same for all instructions except: Branch and Jump







# Single Cycle Datapath for Ori

 

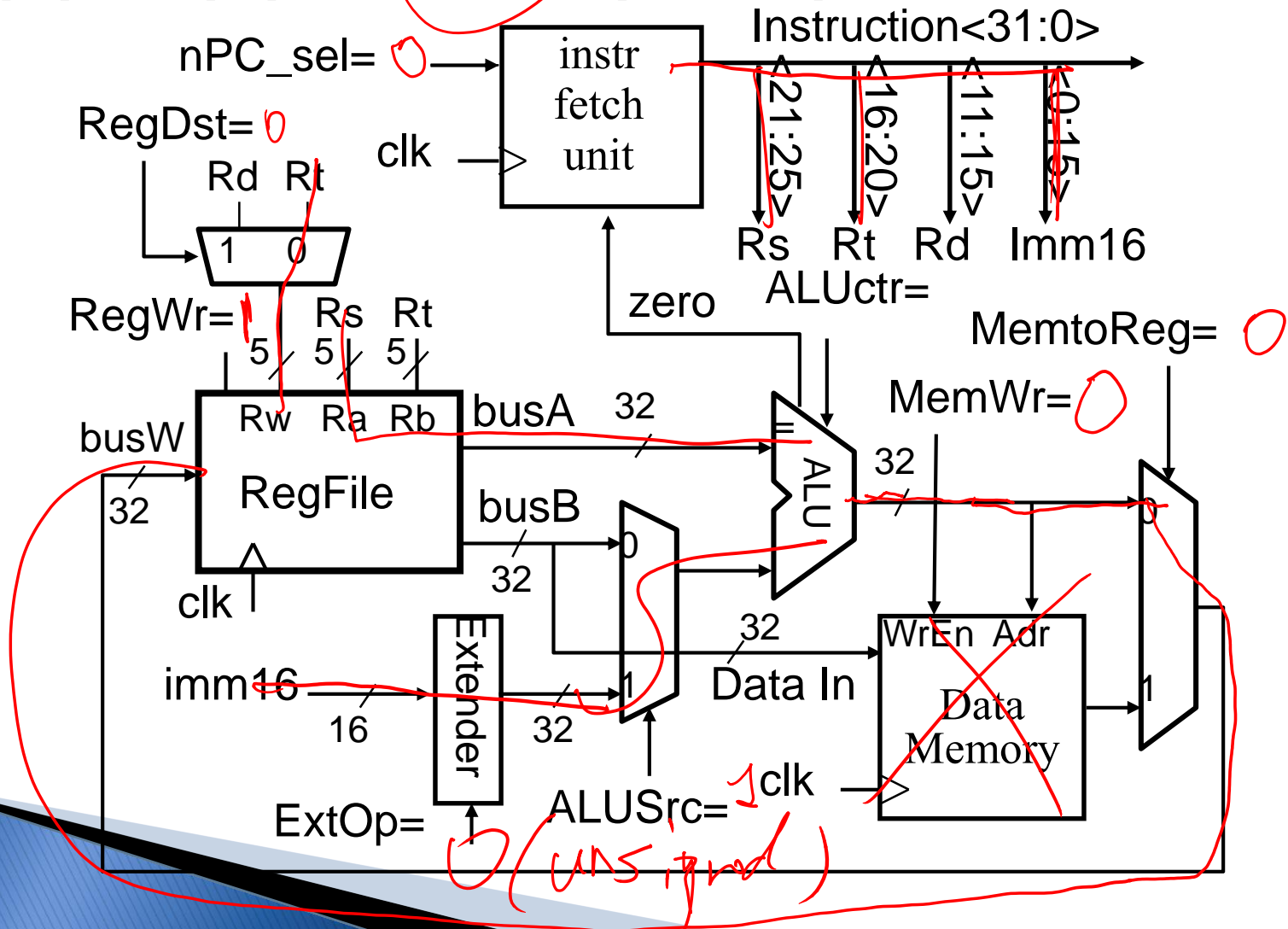
►  $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




# Single Cycle Datapath for Ori

 

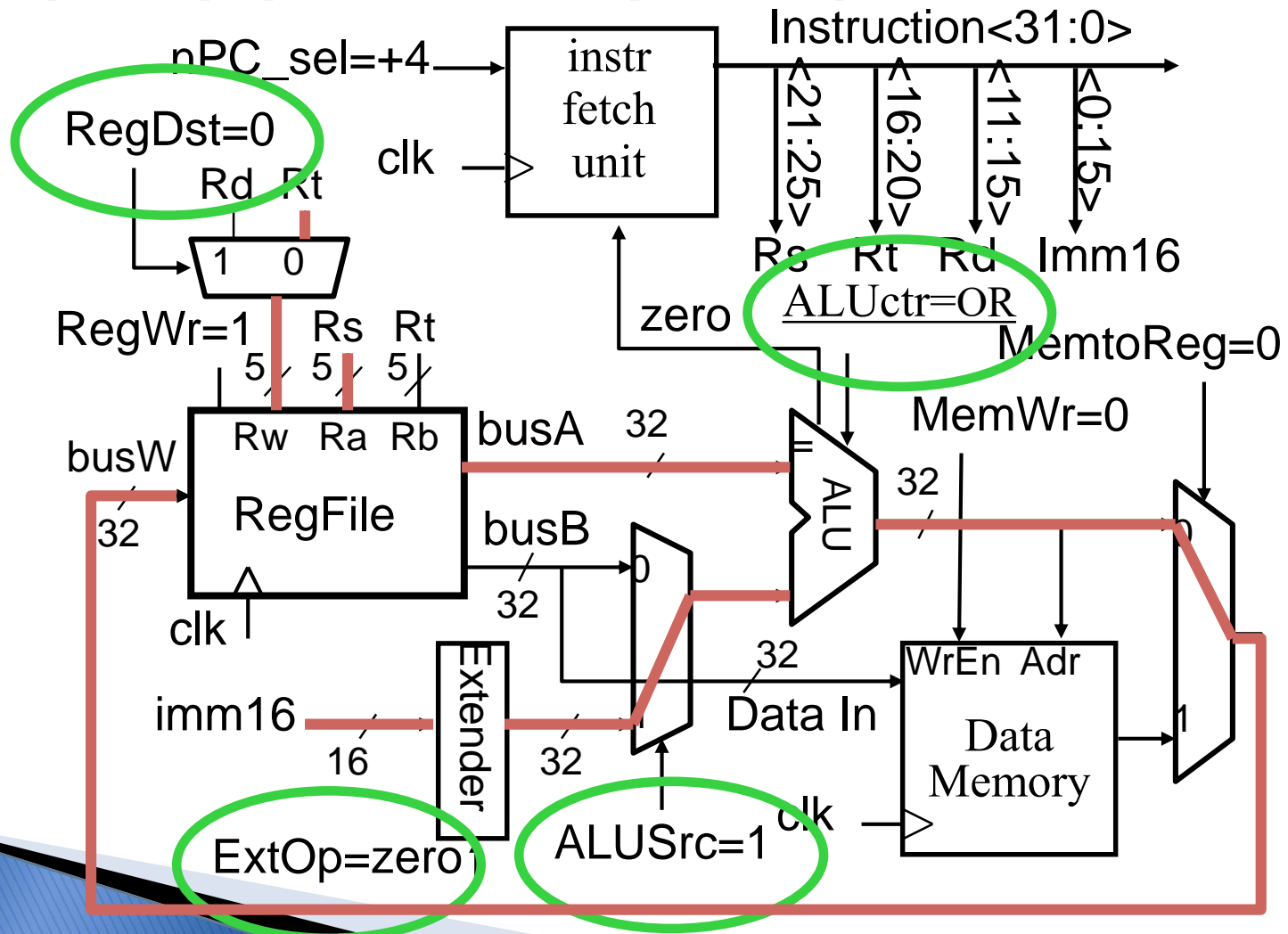
- ▶  $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




# Single Cycle Datapath for LW

 

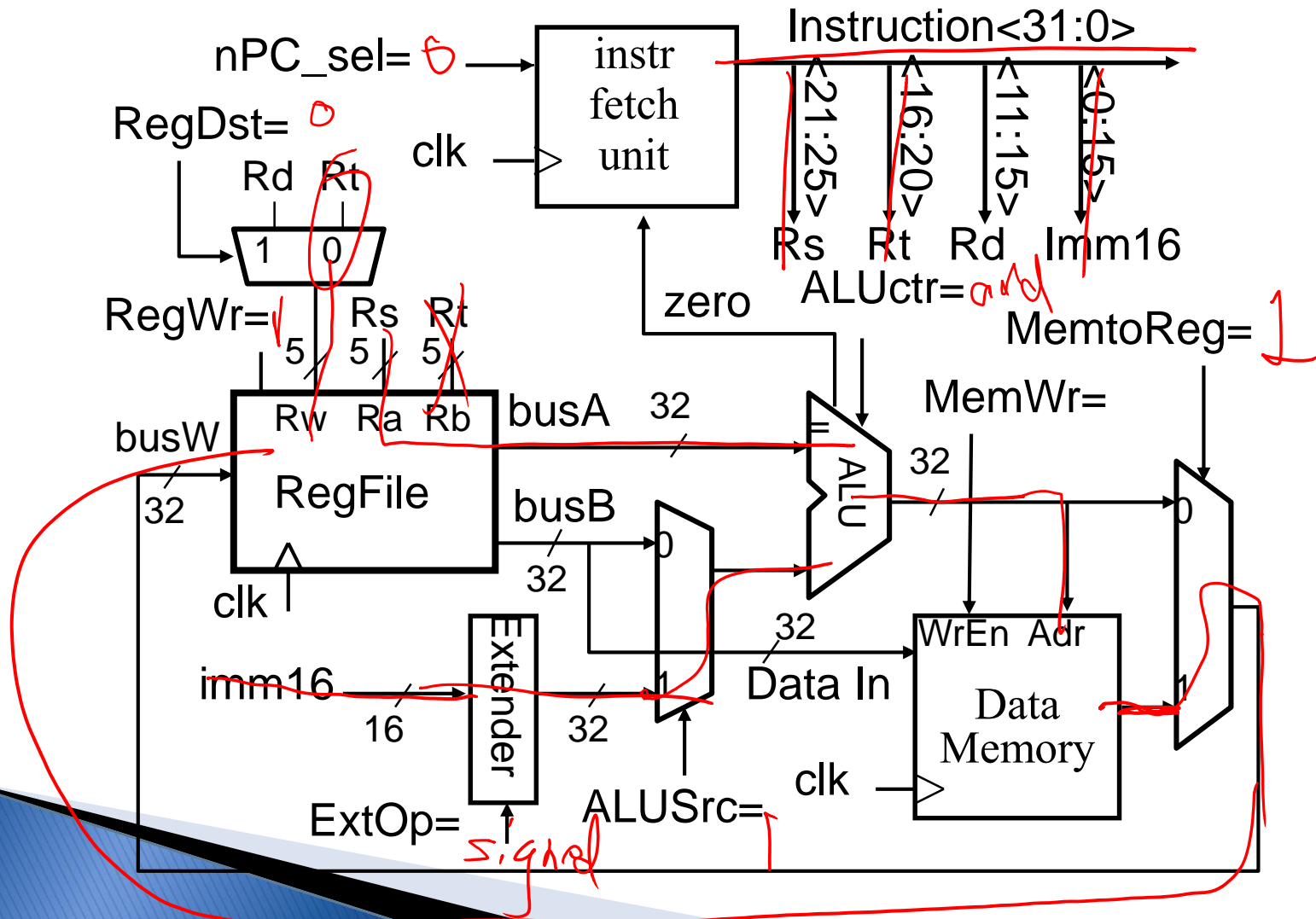
- ▶  $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




# Single Cycle Datapath for LW

 

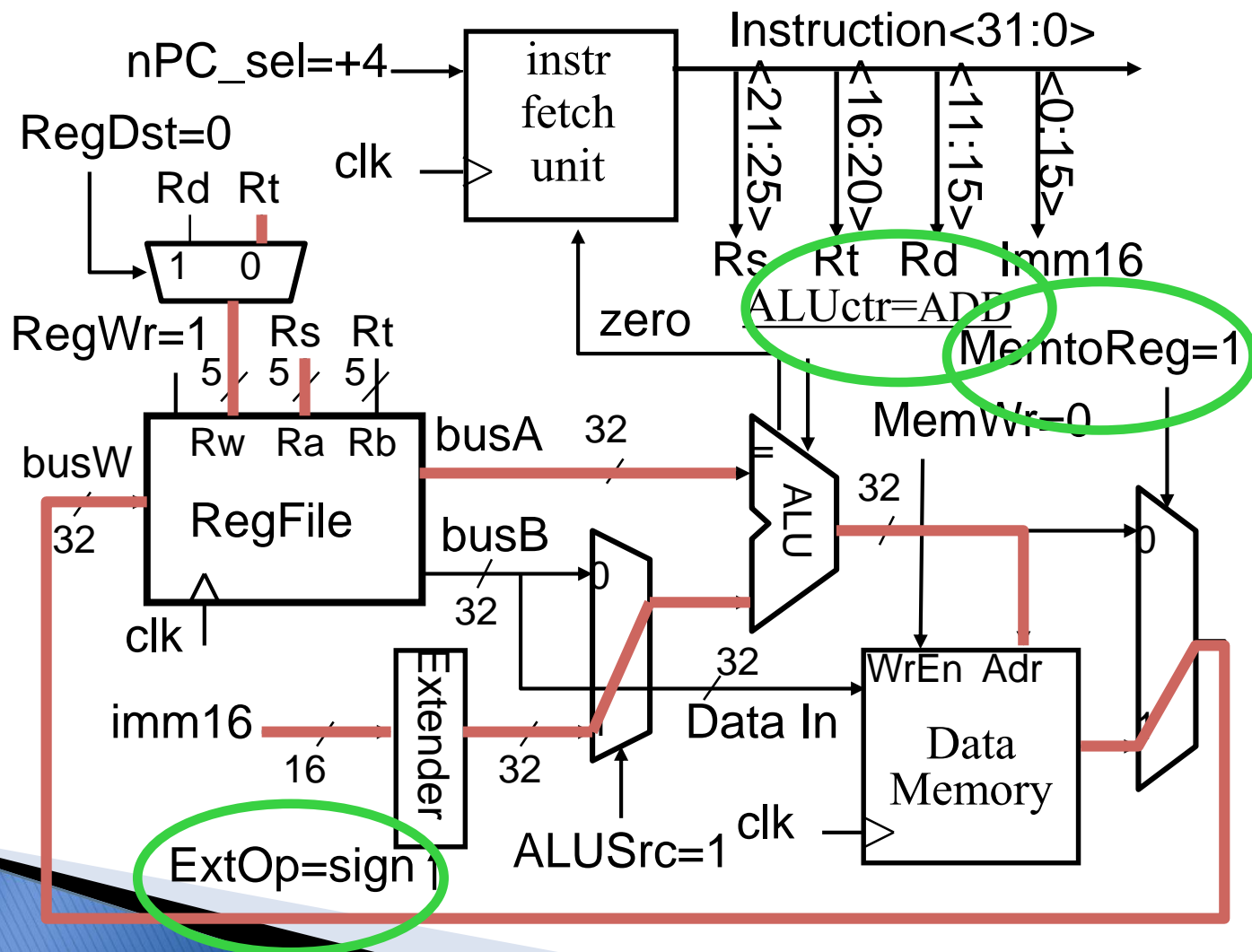
- ▶  $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




# Single Cycle Datapath for SW

 

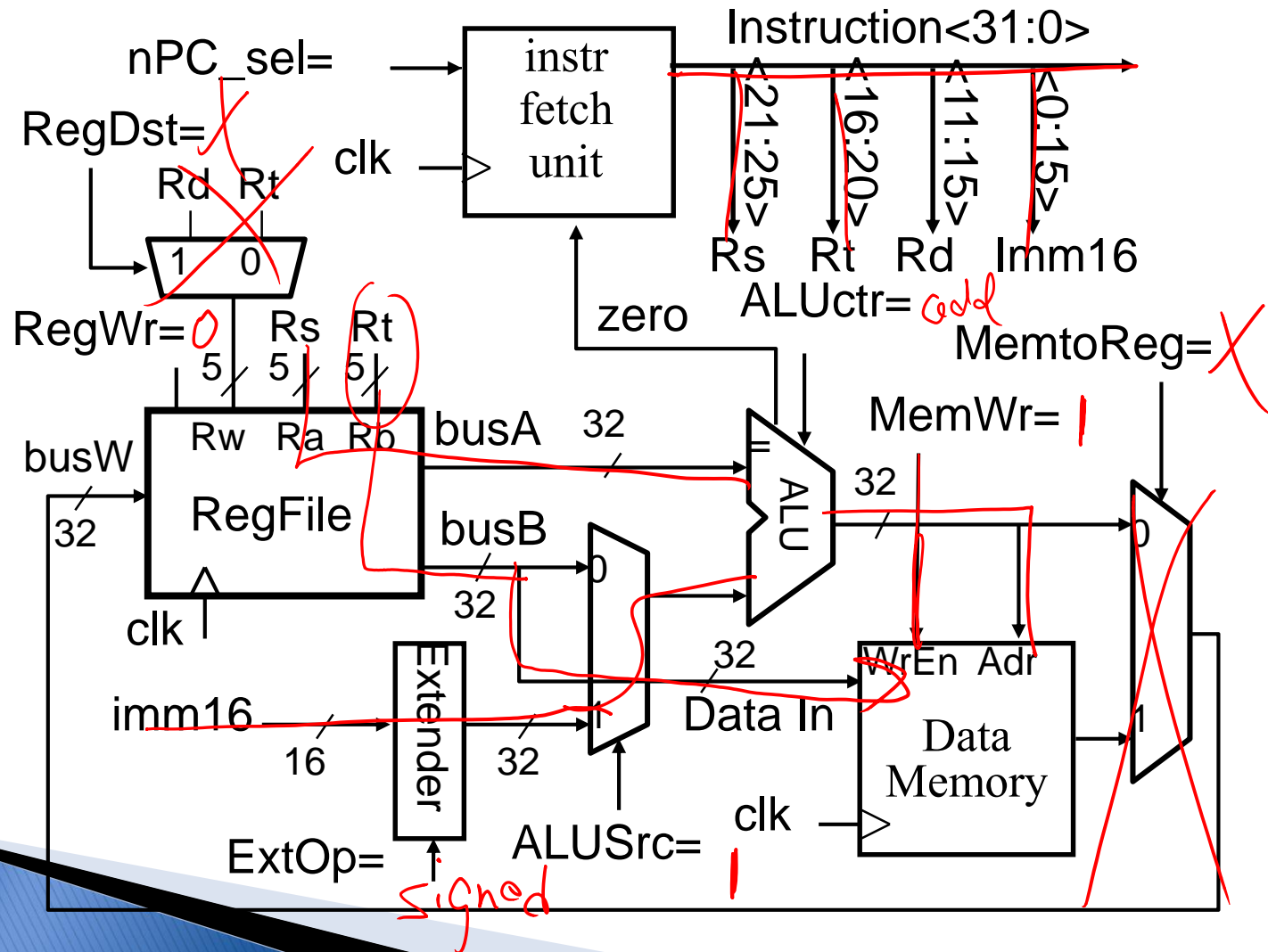
- ▶ Data Memory  $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




# Single Cycle Datapath for SW

 

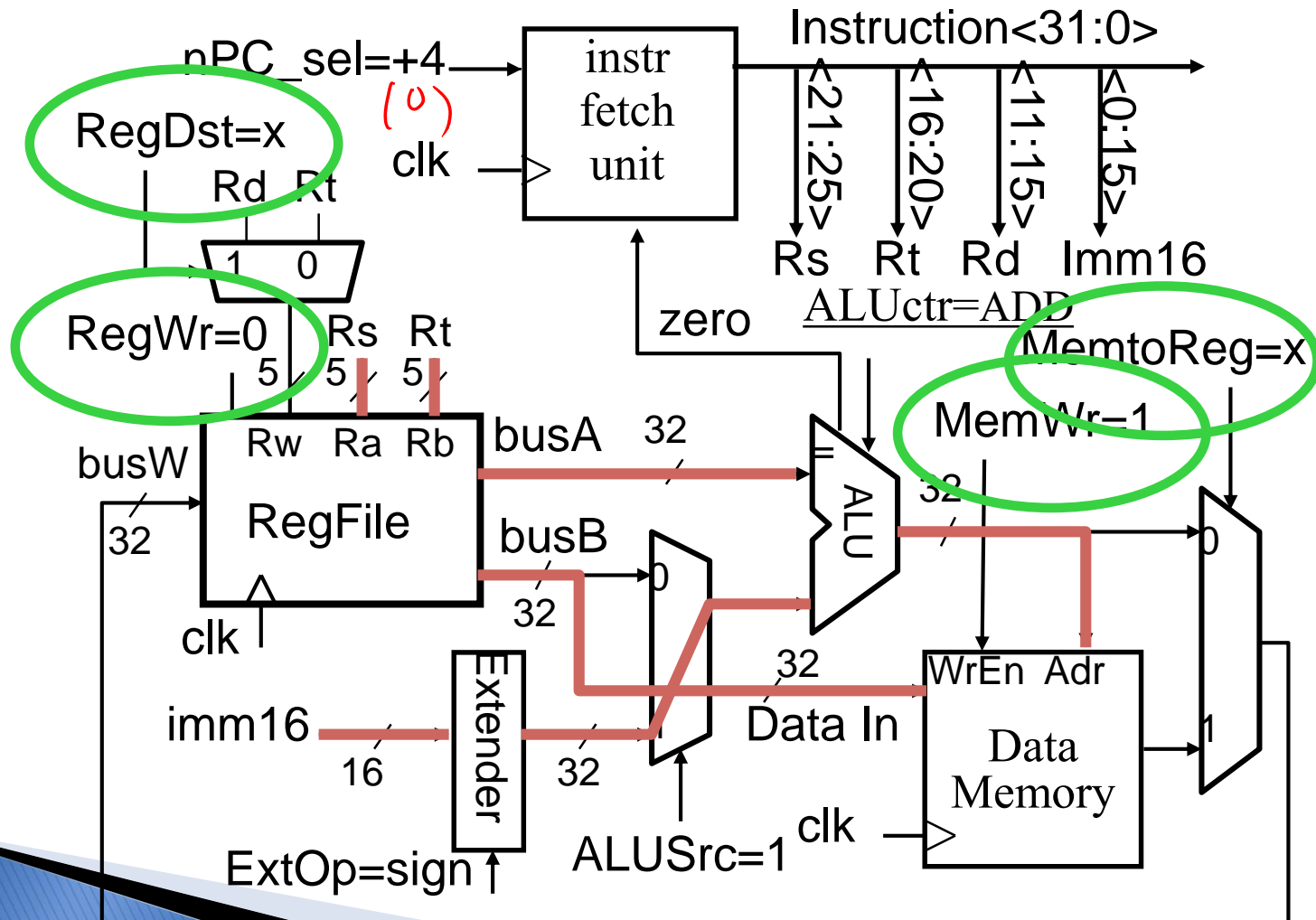- ▶ Data Memory  $\{R[rs] + \text{SignExt}[\text{imm16}]\} = R[rt]$




# Single Cycle Datapath for Branch

 


- ```

▶ if (R[rs] - R[rt] == 0) then Zero = 1 ; else Zero = 0


```

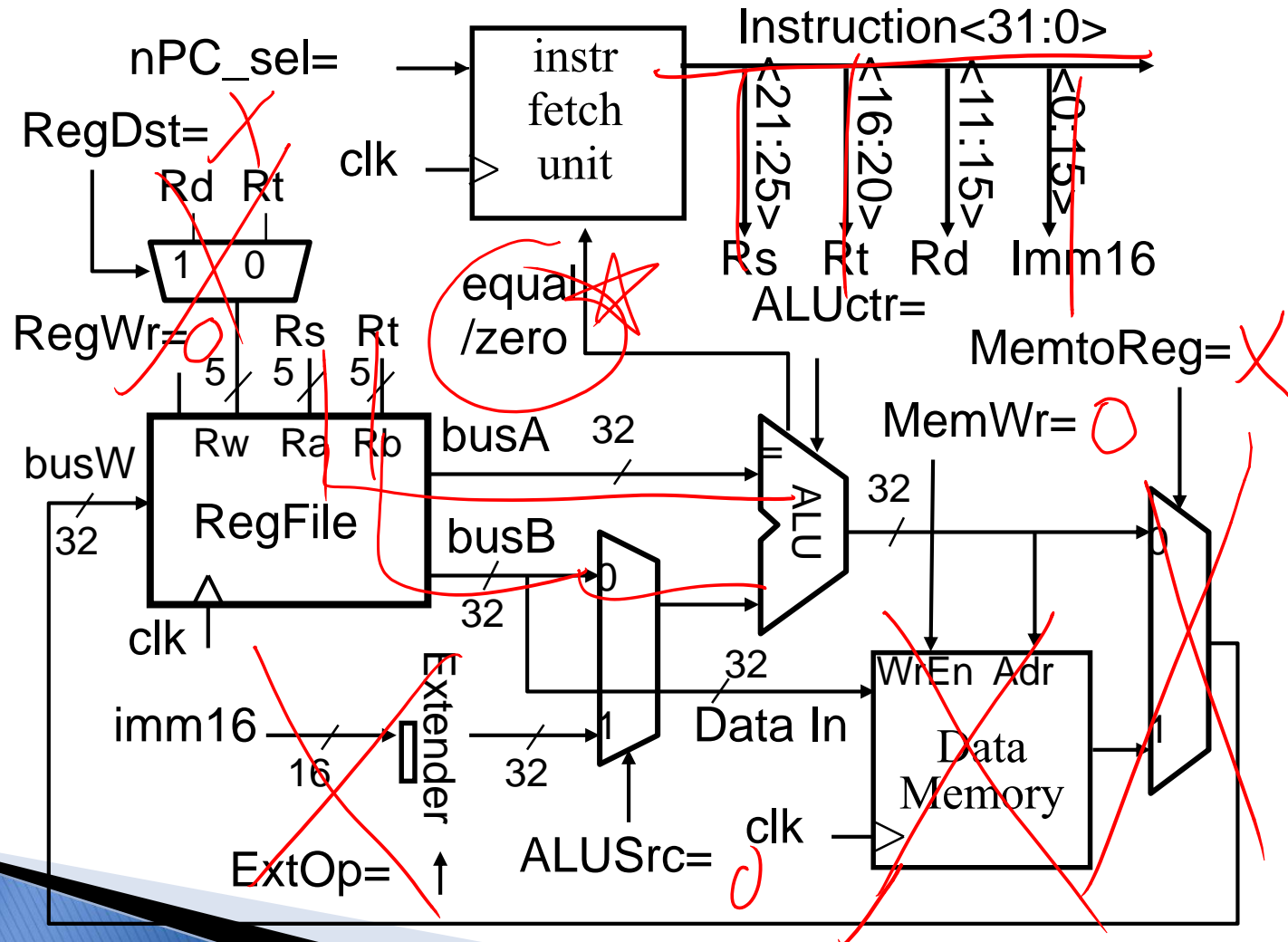

# Single Cycle Datapath for Branch

 


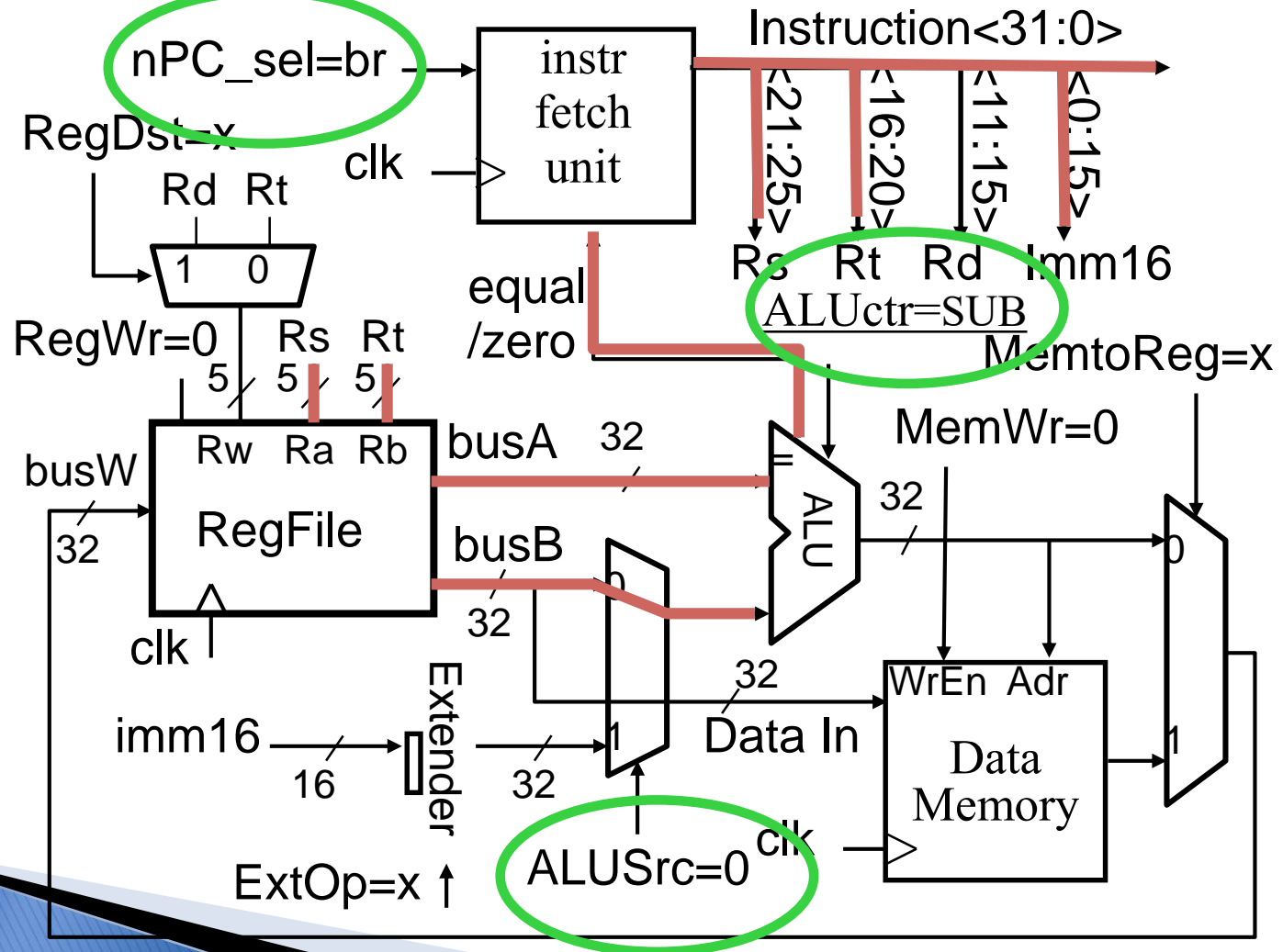- if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0






# Instruction Fetch Unit end of Branch

 

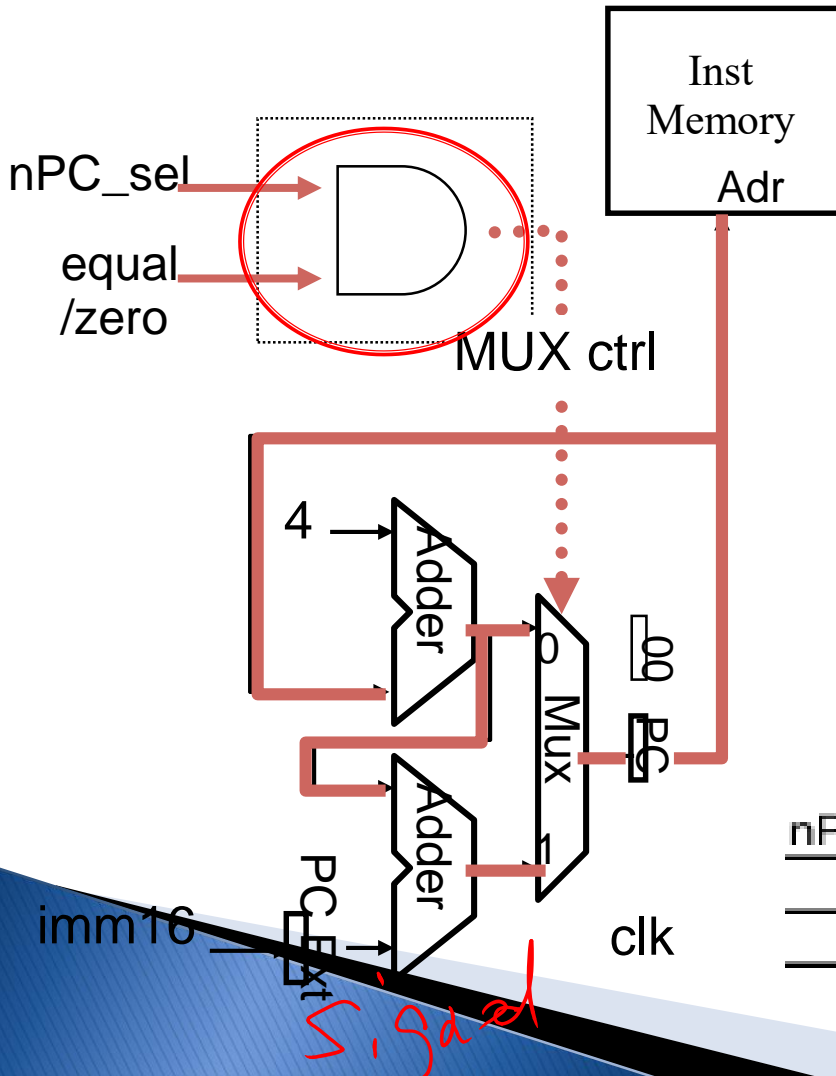- ▶ if (Zero == 1) then  $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$ ; else  $PC = PC + 4$




- What is encoding of `nPC_sel`?
  - **Direct MUX select?**
  - **Branch inst. / not branch**
- Let's pick 2nd option

| <code>nPC_sel</code> | <code>zero?</code> | MUX |
|----------------------|--------------------|-----|
| 0                    | x                  | 0   |
| 1                    | 0                  | 0   |
| 1                    | 1                  | 1   |


Q: What logic gate?




# The Single Cycle Datapath during Jump

 

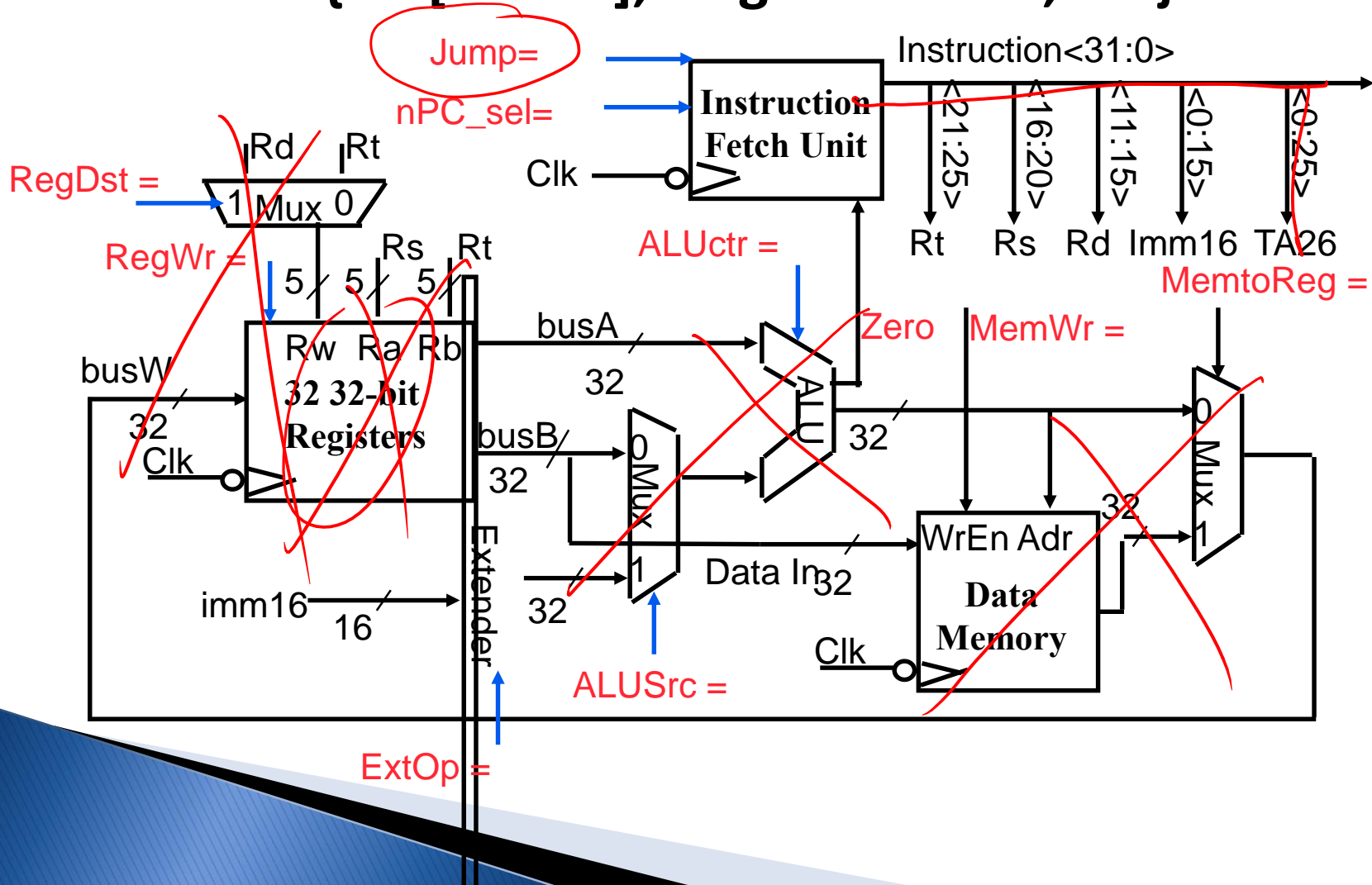
- New PC = { PC[31..28], target address, 00 }




# The Single Cycle Datapath during Jump

 

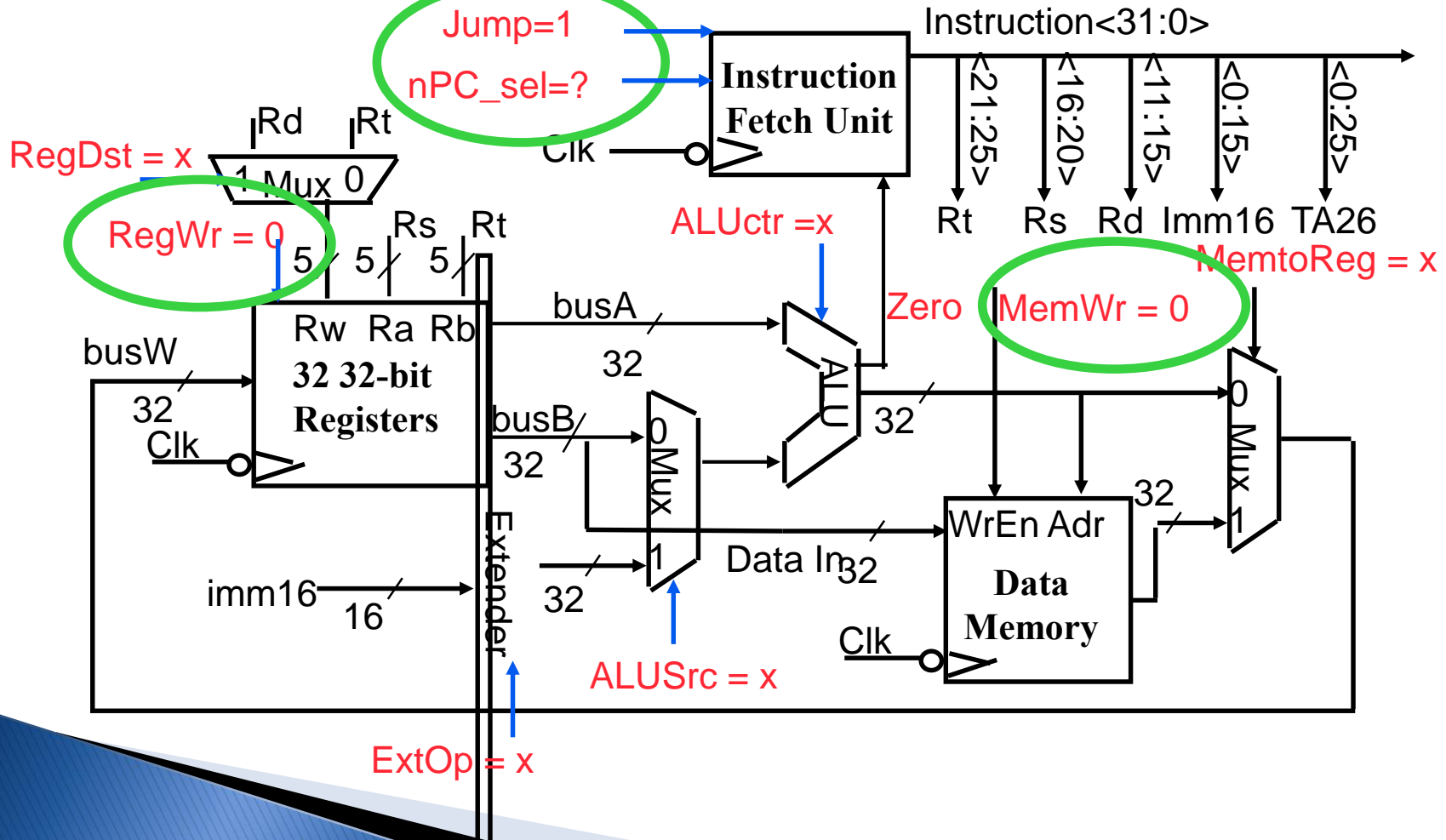
- New PC = { PC[31..28], target address, 00 }


 
# Instruction Fetch Unit at the End of Jump




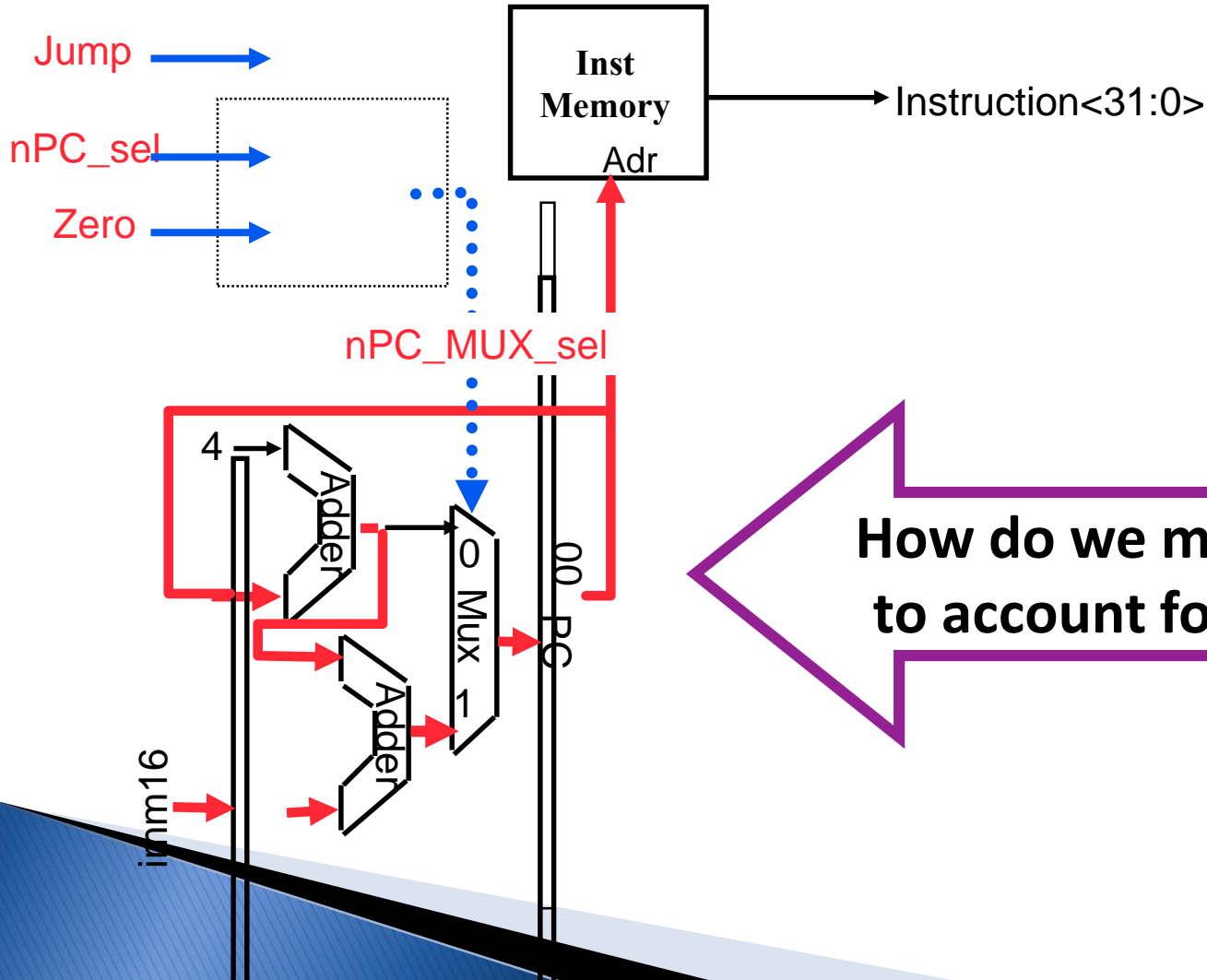- **New PC = { PC[31..28], target address, 00 }**




How do we modify this to account for jumps?
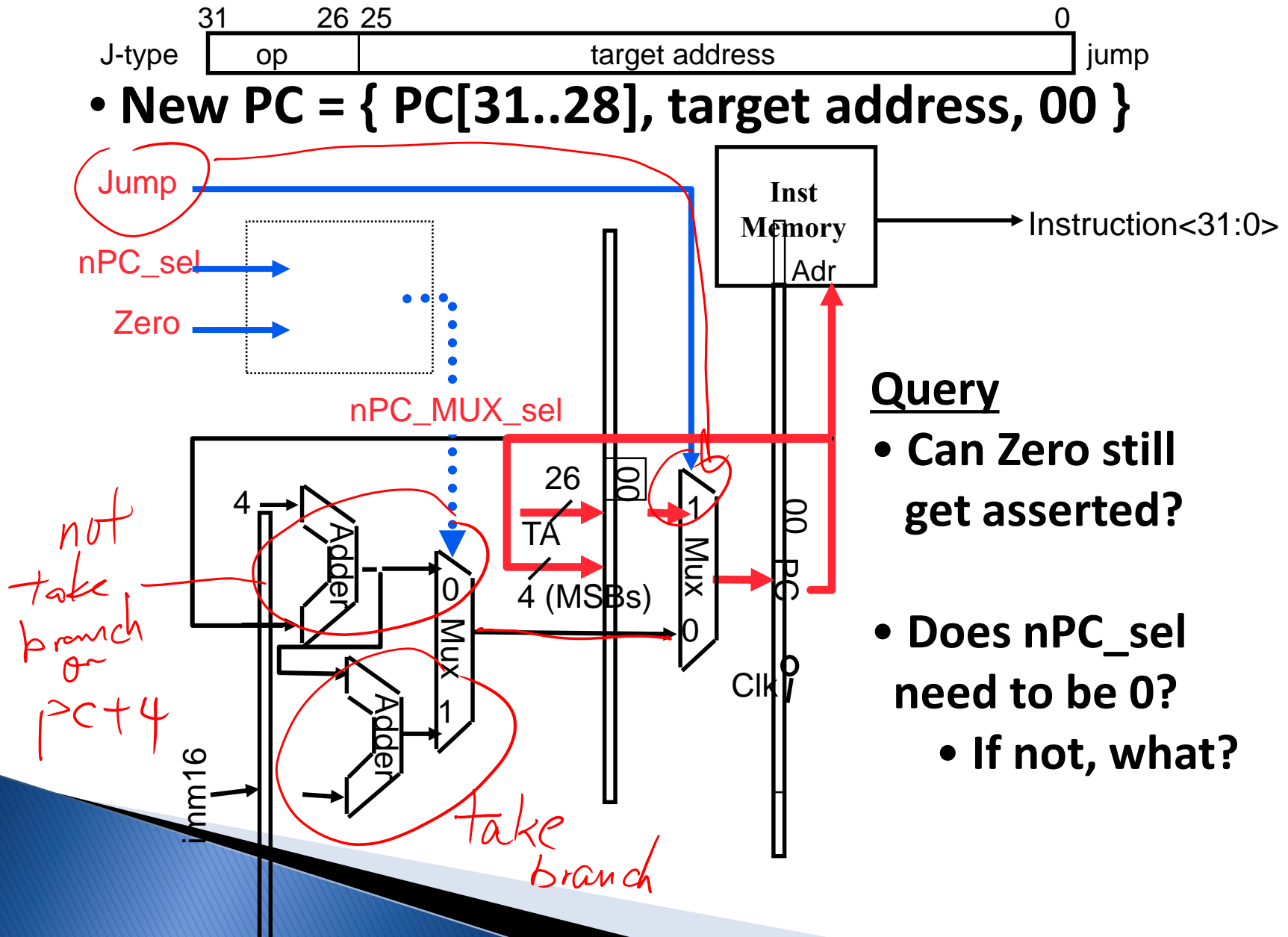
## Instruction Fetch Unit at the End of Jump



# Quiz

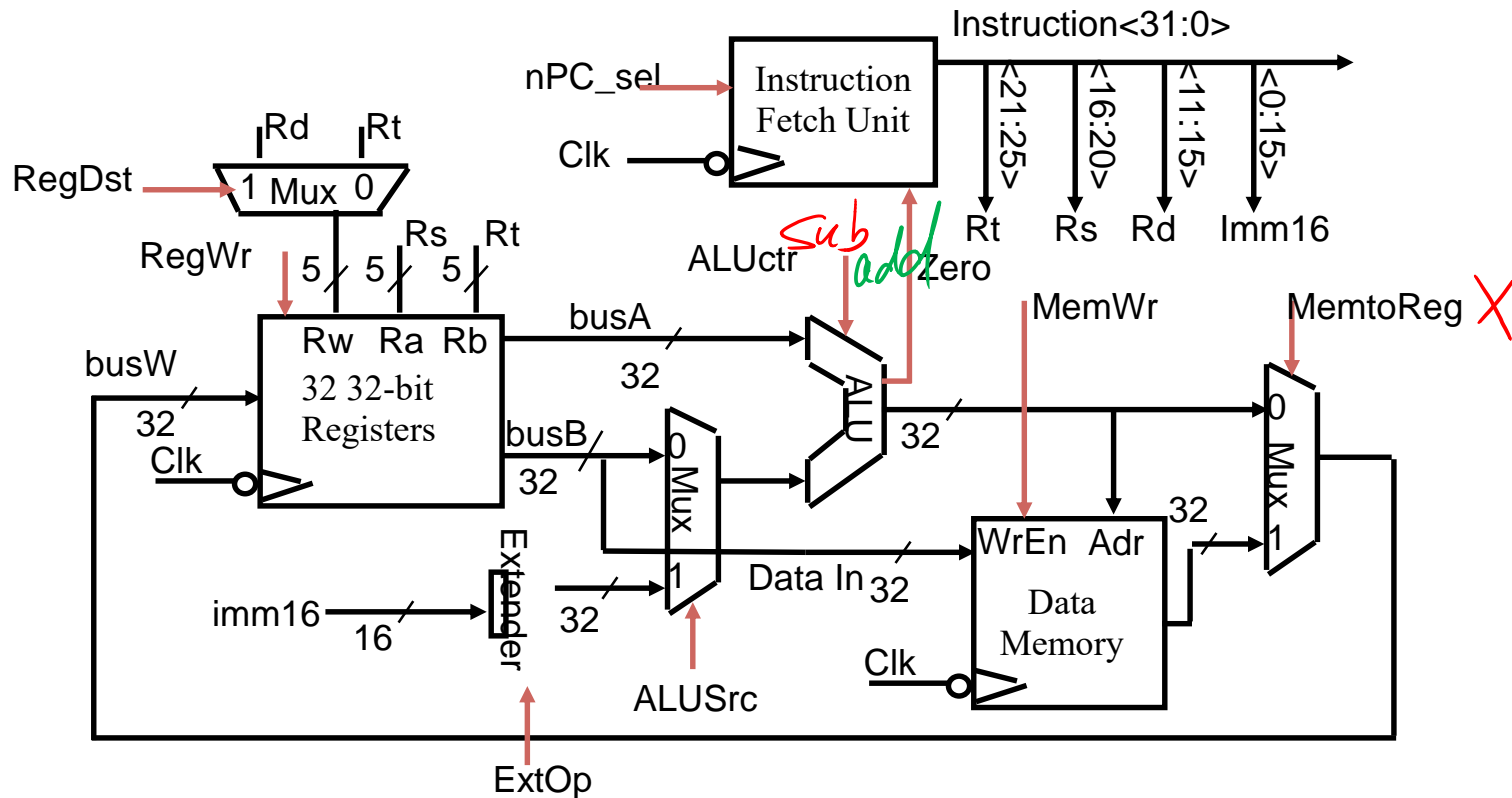


- 1) MemToReg='x' & ALUctr='sub'.  
SUB or BEQ?
- 2) ALUctr='add'. Which 1 signal is different for all 3 of:  
ADD, LW, & SW? RegDst or ExtOp?

*LD, X, S, Y*

|    |    |
|----|----|
|    | 12 |
| a) | SR |
| b) | SE |
| c) | BR |
| d) | BE |

# Quiz

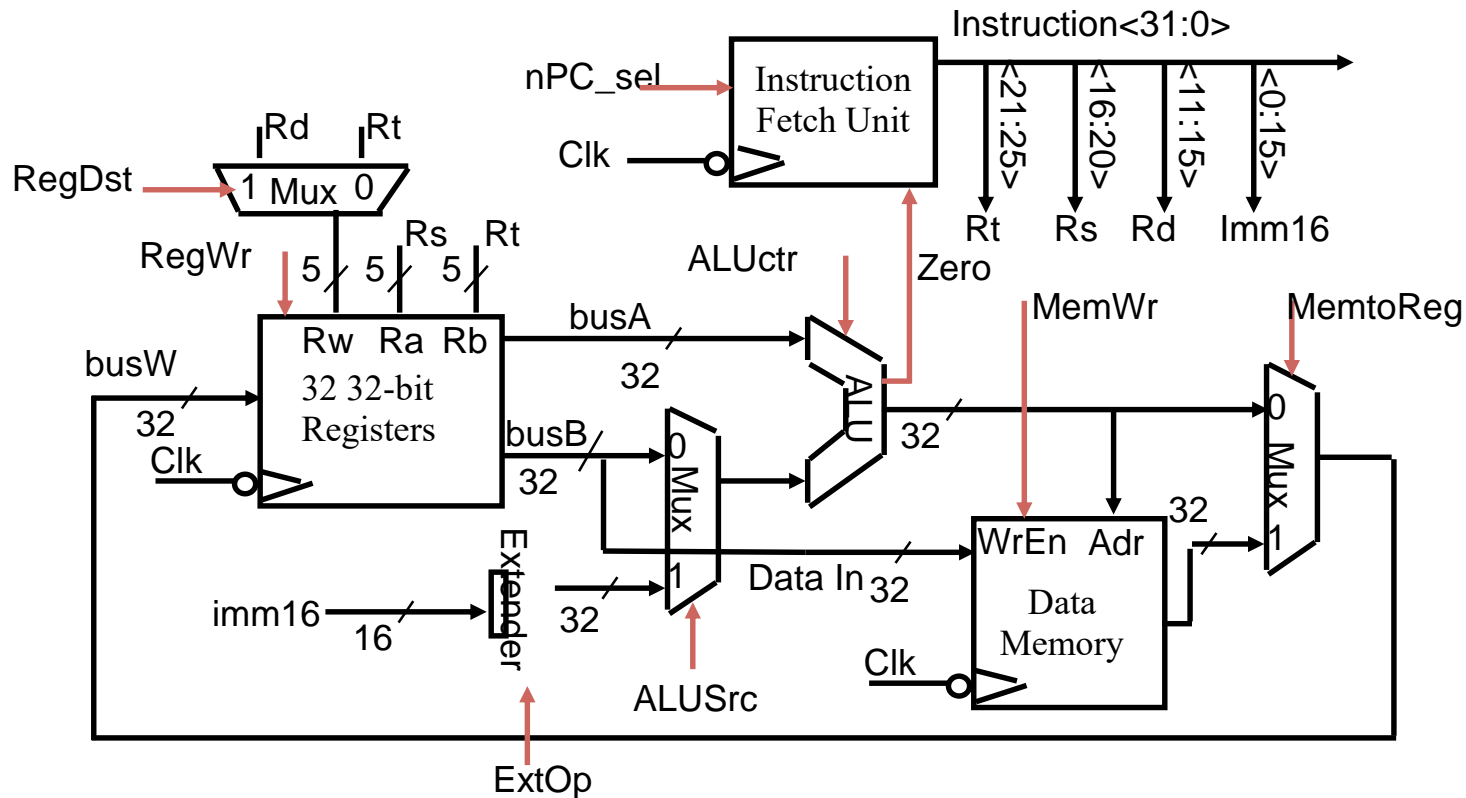

- 1) MemToReg='x' & ALUctr='sub'.  
SUB or BEQ?
- 2) ALUctr='add'. Which 1 signal is different for all 3 of:  
ADD, LW, & SW? RegDst or ExtOp?

|           |           |
|-----------|-----------|
|           | 12        |
| a)        | SR        |
| b)        | SE        |
| <b>c)</b> | <b>BR</b> |
| d)        | BE        |

# Summary: Single-cycle Processor

- 5 steps to design a processor
  - 1. Analyze instruction set → datapath requirements
  - 2. Select set of datapath components & establish clock methodology
  - 3. Assemble datapath meeting the requirements
  - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
  - 5. Assemble the control logic
    - Formulate Logic Equations
    - Design Circuits

