

CSE 31

Computer Organization

Lecture 23 – CPU Design (2)

Announcement

- ▶ No lab this week
 - Project #1 grading during lab
- ▶ HW #7 at zyBooks
 - Due Monday(12/10) at 11:59pm
- ▶ Project #2
 - Due Monday (12/3)
 - Don't start late, you won't have time!
- ▶ Course evaluation online
 - Fill out by 12/6 (Thursday)
- ▶ Reading assignment
 - Chapter 5.7 – 5.11 of zyBooks (Reading Assignment #6)
 - Make sure to do the Participation Activities
 - Due Wednesday (12/5)

Announcement


► Final Exam

- 12/11 (Tuesday), 11:30 – 2:30pm
- Cover all
- Practice exam in CatCourses
- Closed book
- 2 sheet of note (8.5" x 11")
- MIPS reference sheet will be provided
- Review: 12/10 (Monday) 1-3pm, COB 113

Review


- ▶ CPU design involves Datapath, Control
 - Datapath in MIPS involves 5 CPU stages
 1. Instruction Fetch
 2. Instruction Decode & Register Read
 3. ALU (Execute)
 4. Memory
 5. Register Write

Generic Steps of Datapath

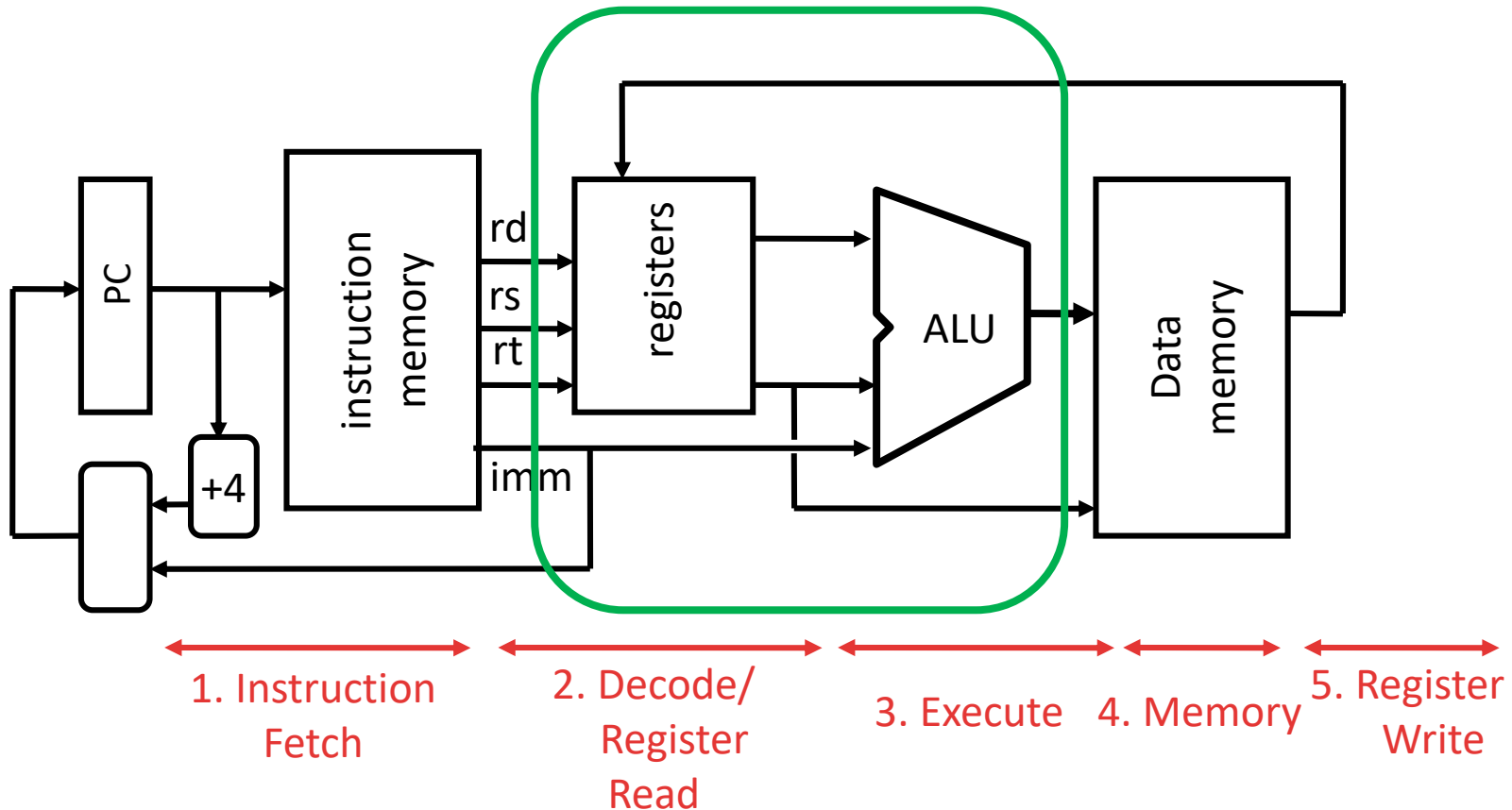


How do we handle the different register usage between r-type and i-type instructions?


Data Multiplexor (mux) (2-to-1, n-bits)

 

4-to-1 Multiplexor?

 


A zoomed in version of RegFile and ALU

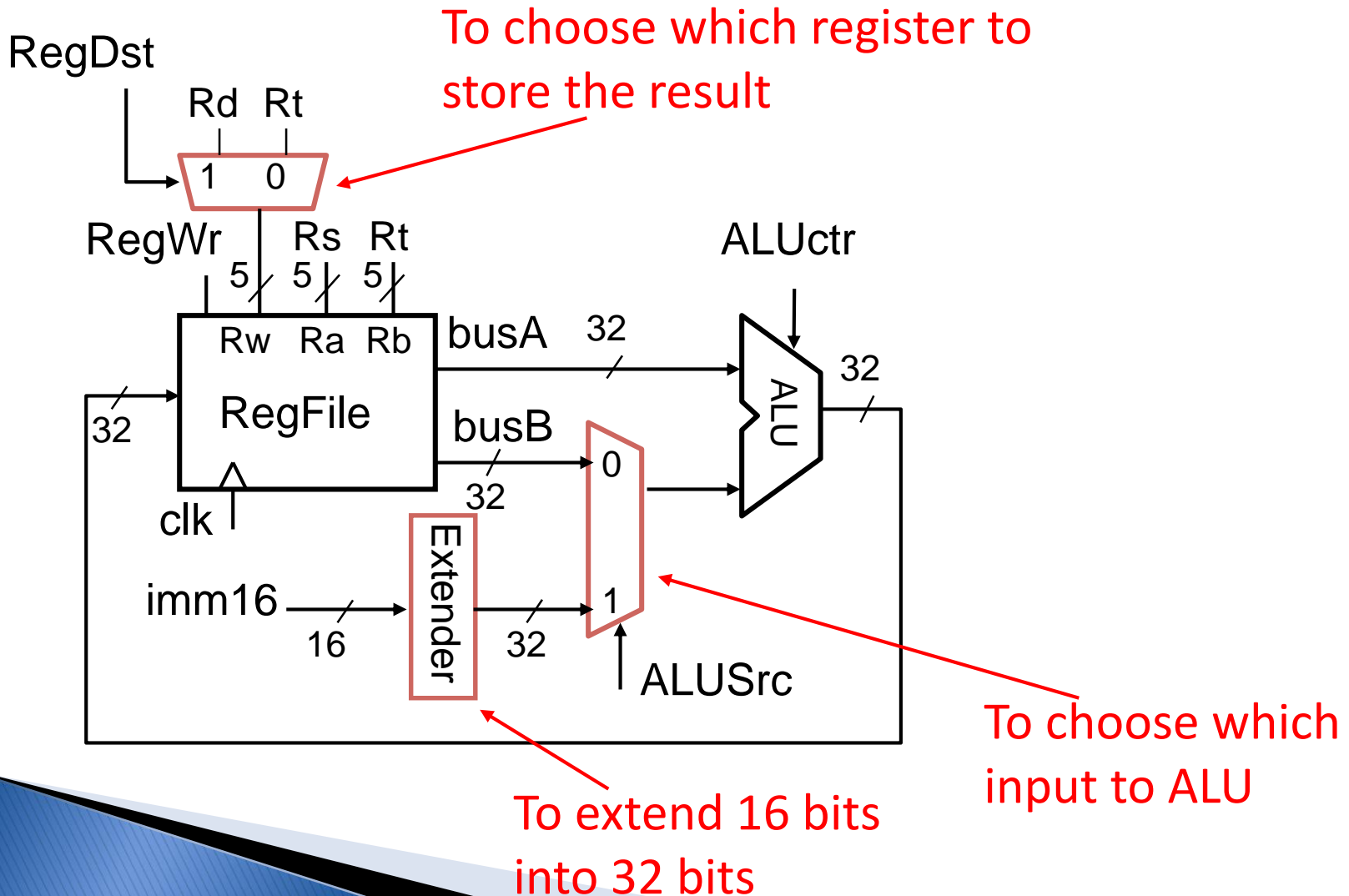


Operations with Immediate

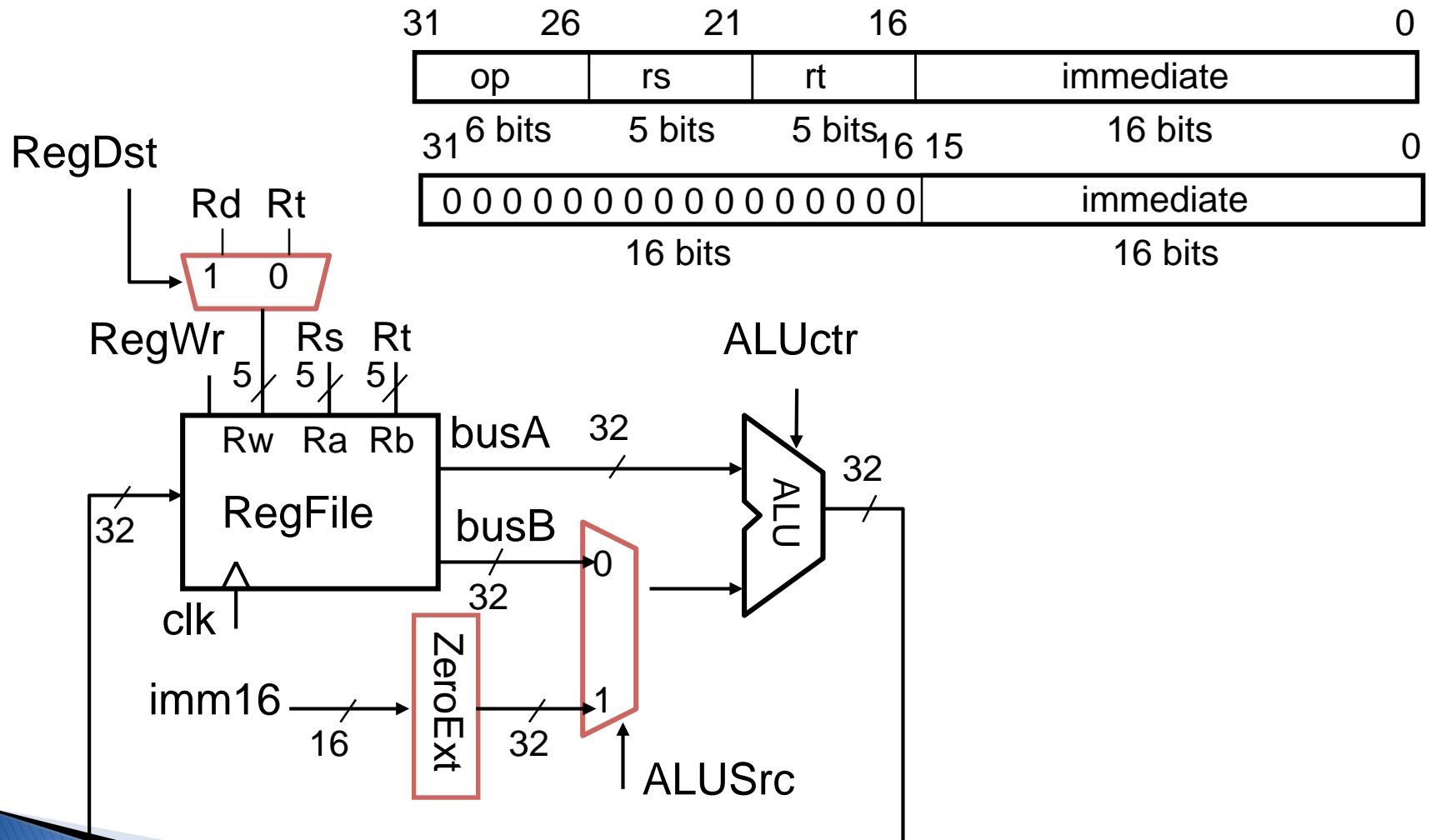- ▶ $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$



Operations with Immediate

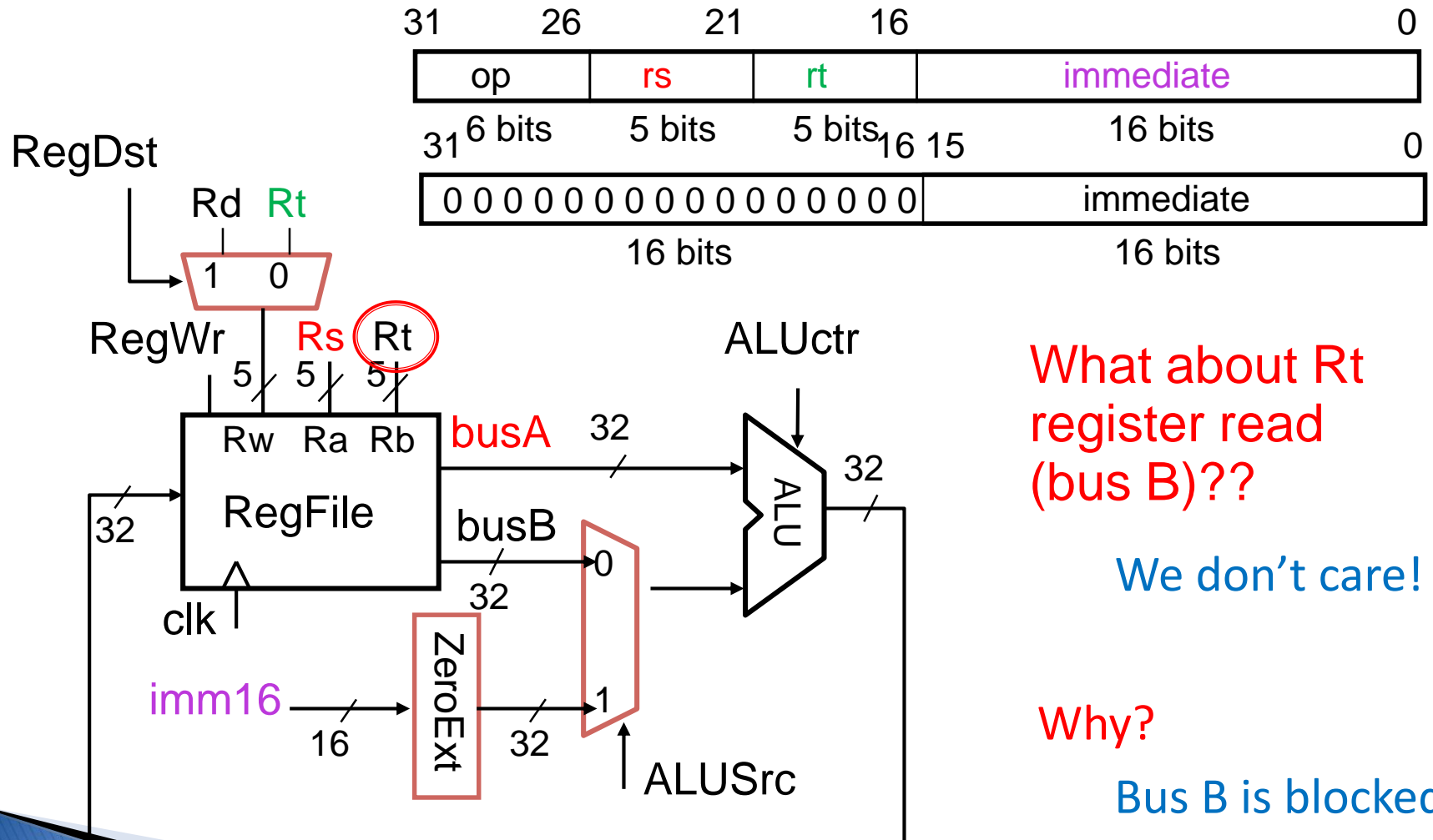- ▶ $R[\text{rt}] = R[\text{rs}] \text{ op ZeroExt}[\text{imm16}]$



What about Rt
register read
(bus B)??


We don't care!

Why?

Bus B is blocked

Load Memory

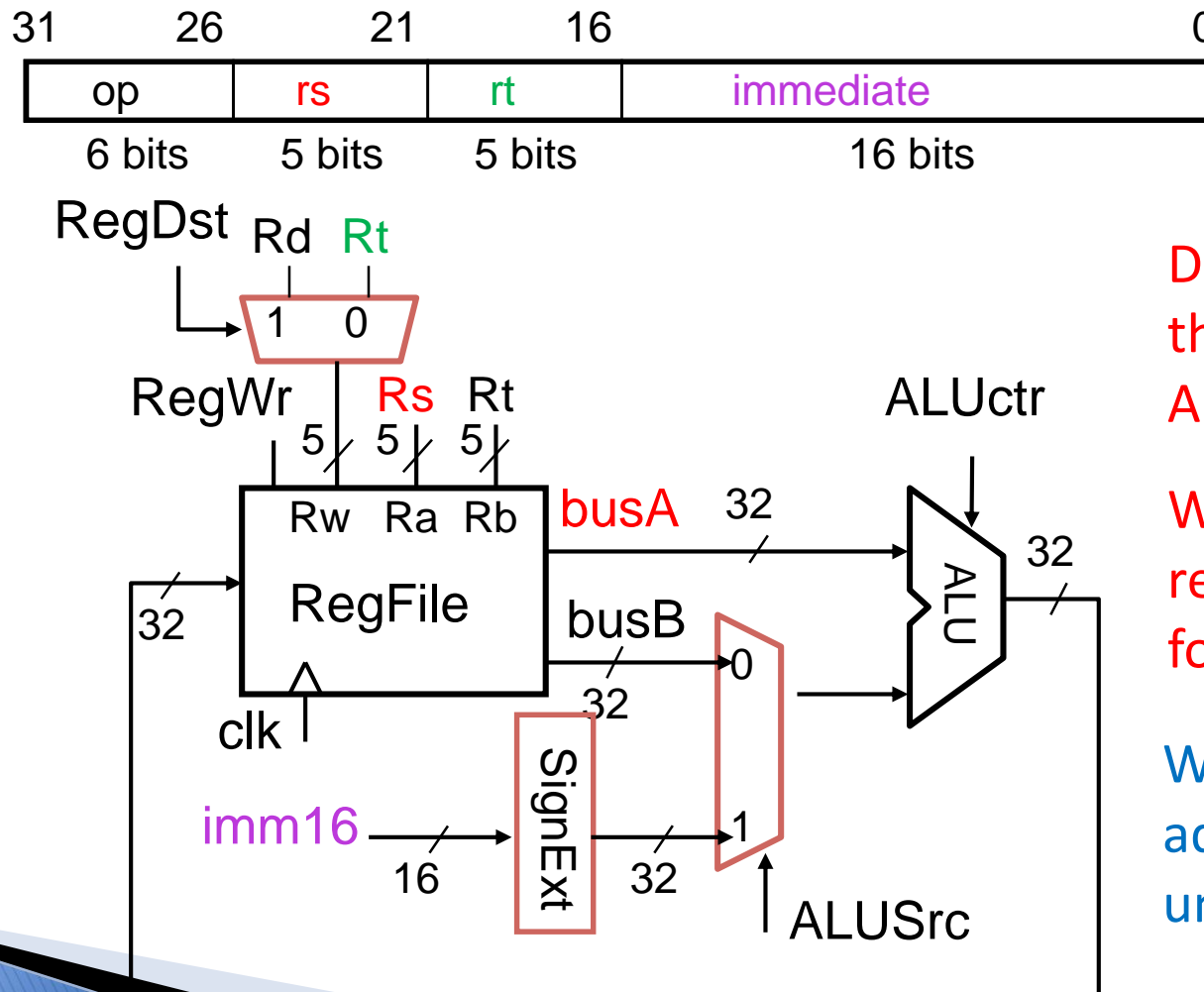- ▶ $R[\underline{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$
- ▶ Example: `lw rt, rs, imm16`



Do we store
the result of
ALU?


What is the
result of ALU
for?

We need to
add a memory
unit!

Load Memory

► $R[\underline{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$

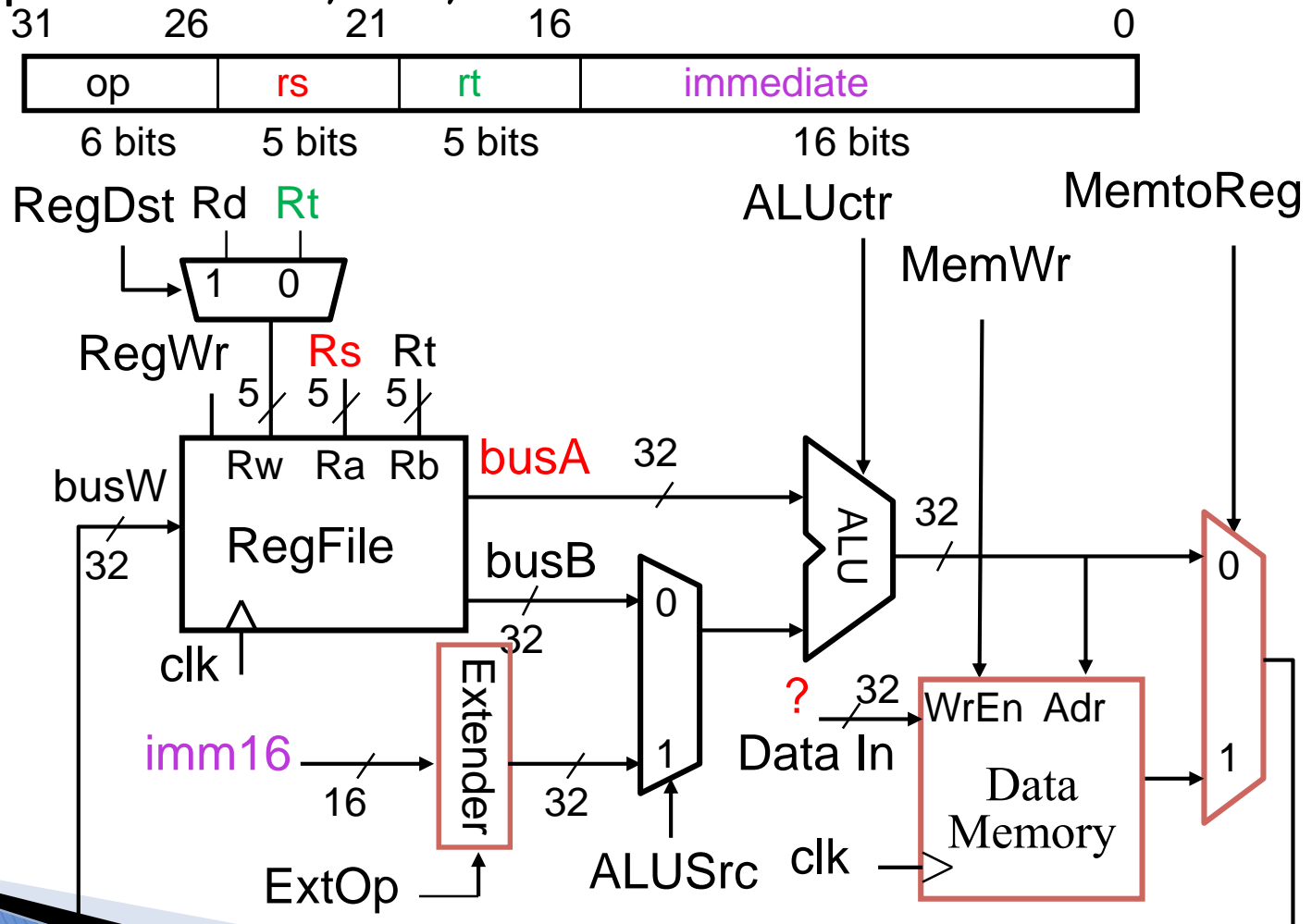
► Example: $\text{lw } rt, rs, \text{imm16}$



Store Memory

- ▶ $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] = \text{R}[\text{rt}]$


Ex.: `sw rt, rs, imm16`

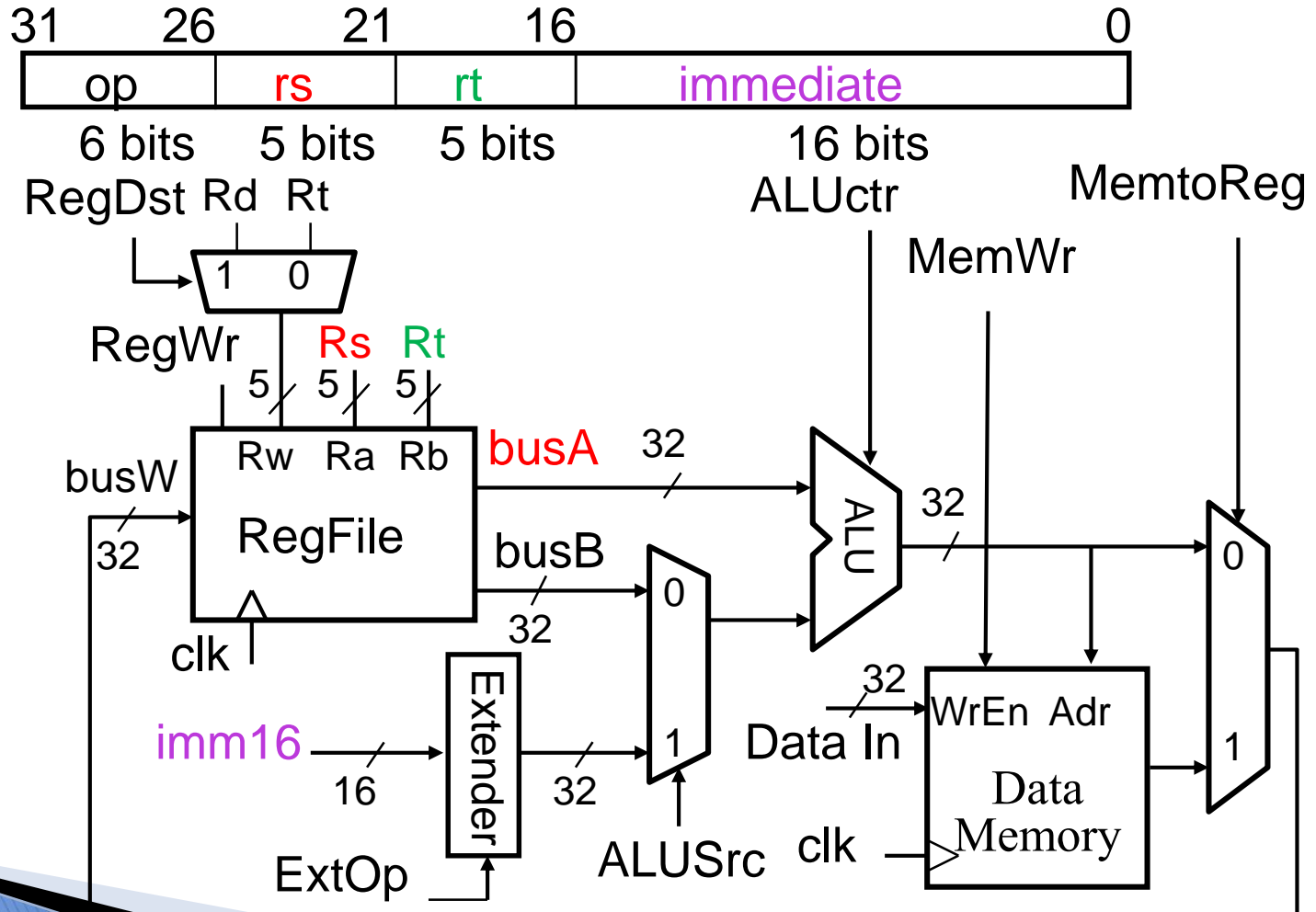

Store Memory

- ▶ $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] = \text{R}[\text{rt}]$



Ex.: `sw rt, rs, imm16`

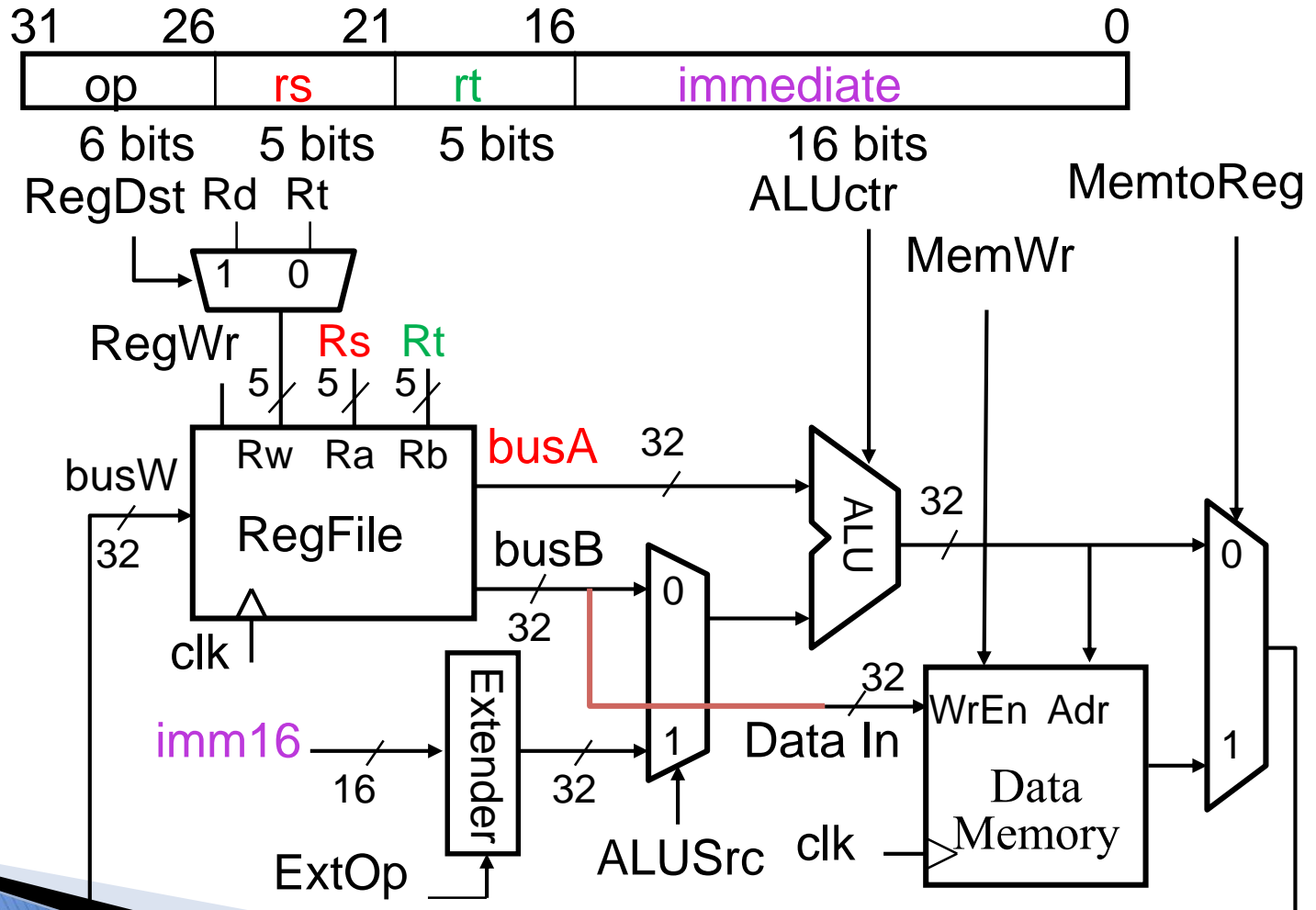

Datapath for Branch Operations

- ▶ beq rs, rt, imm16


Datapath generates condition (equal)

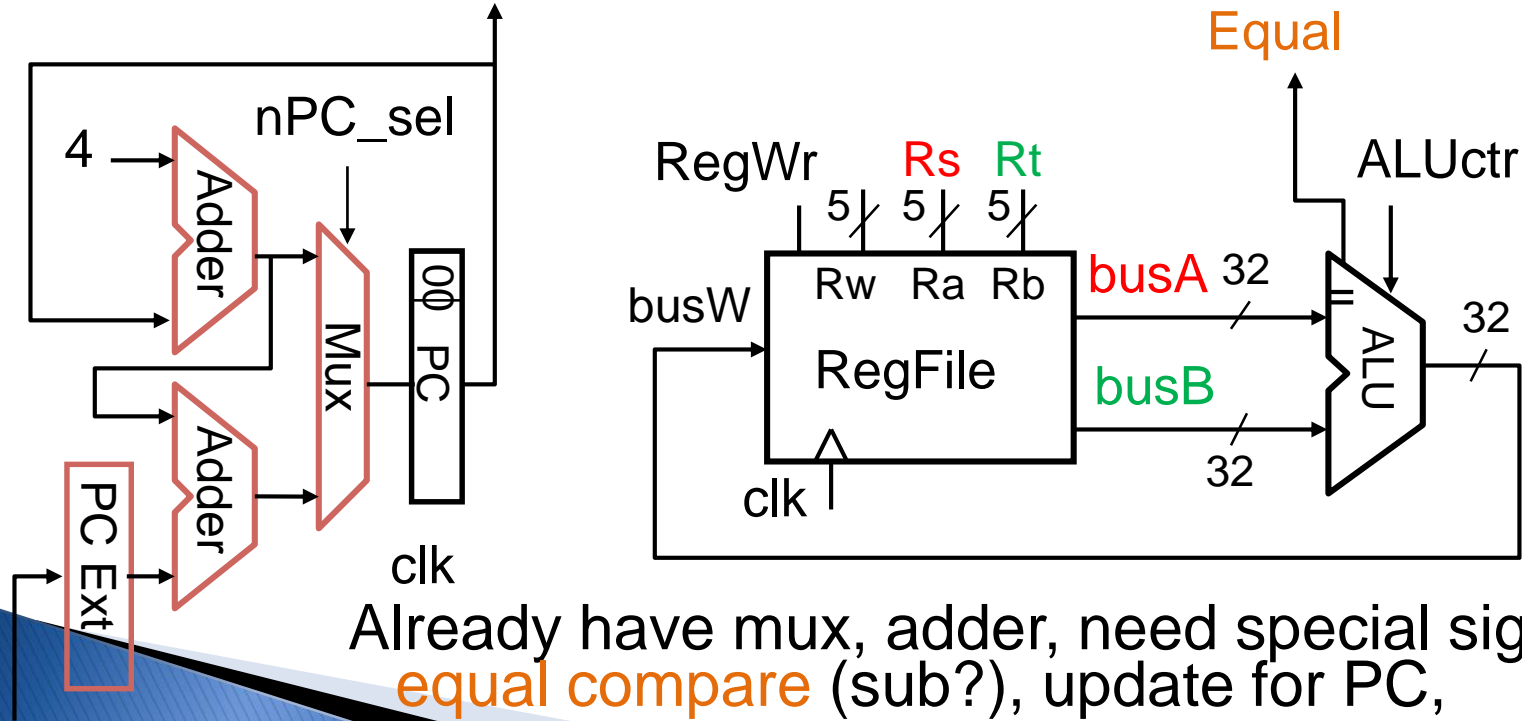 


Already have mux, adder, need special sign need
equal compare (sub?), update for PC,

imm16

Single Cycle Datapath

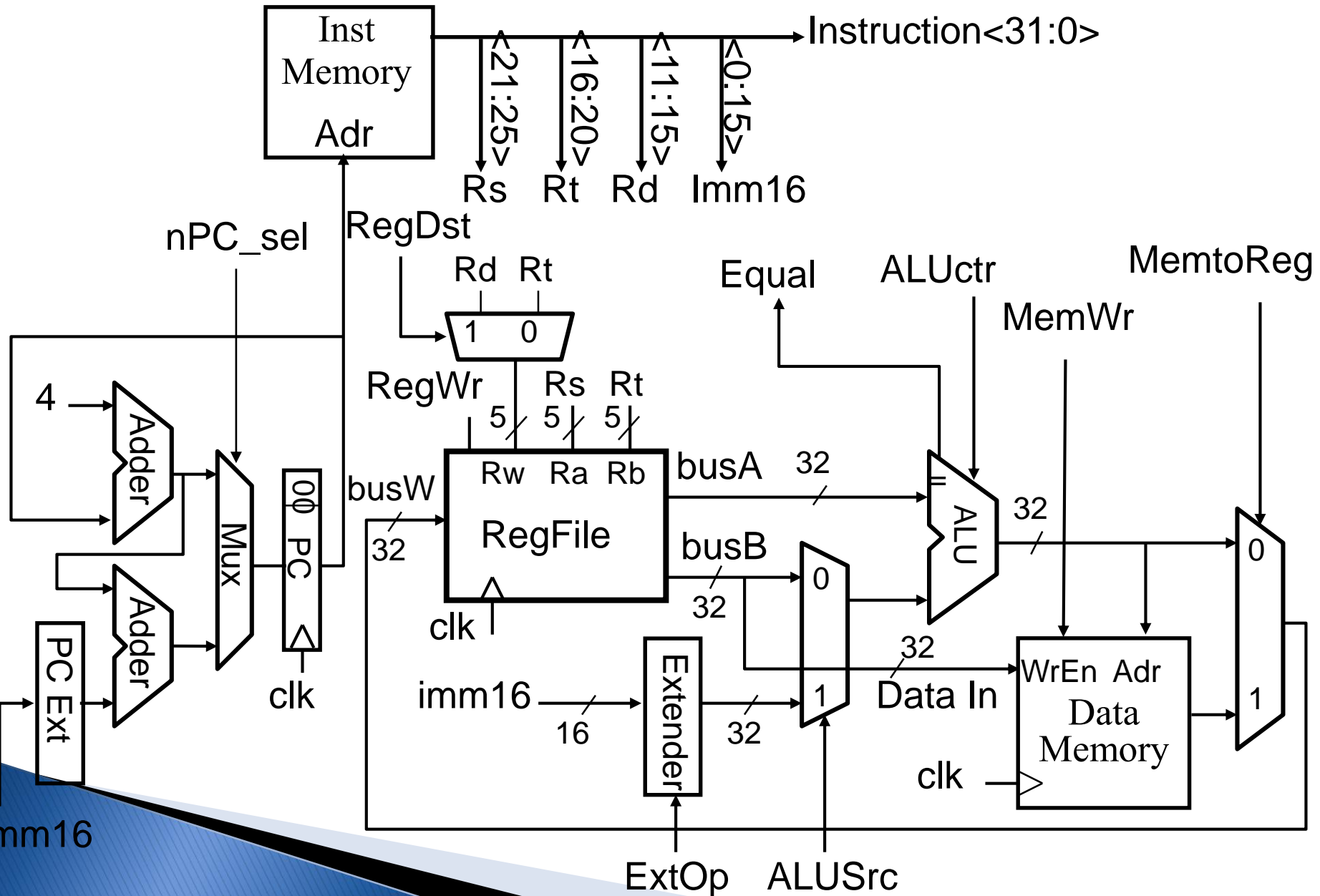


Abstract View of the Implementation

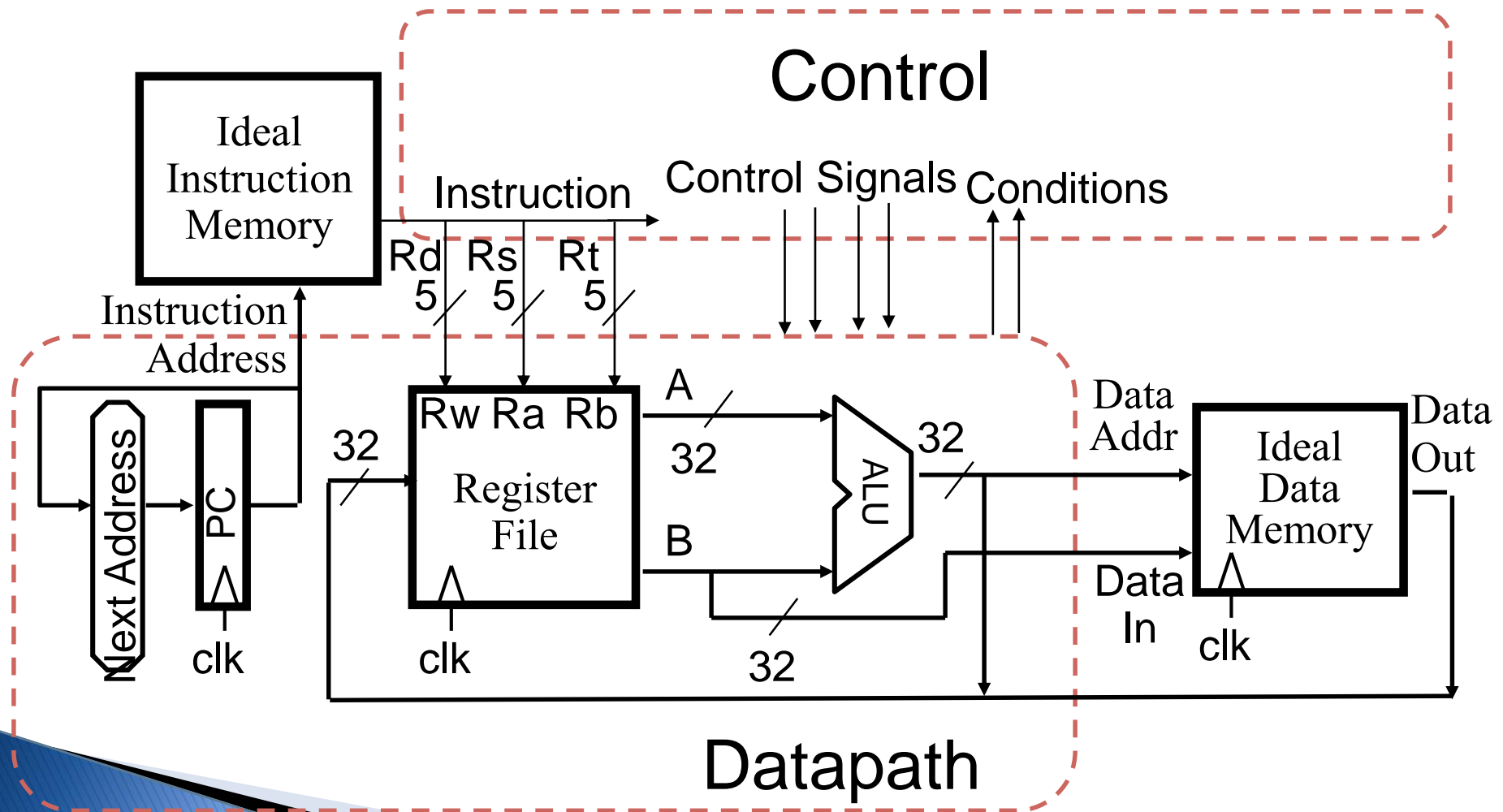

A Single Cycle Datapath

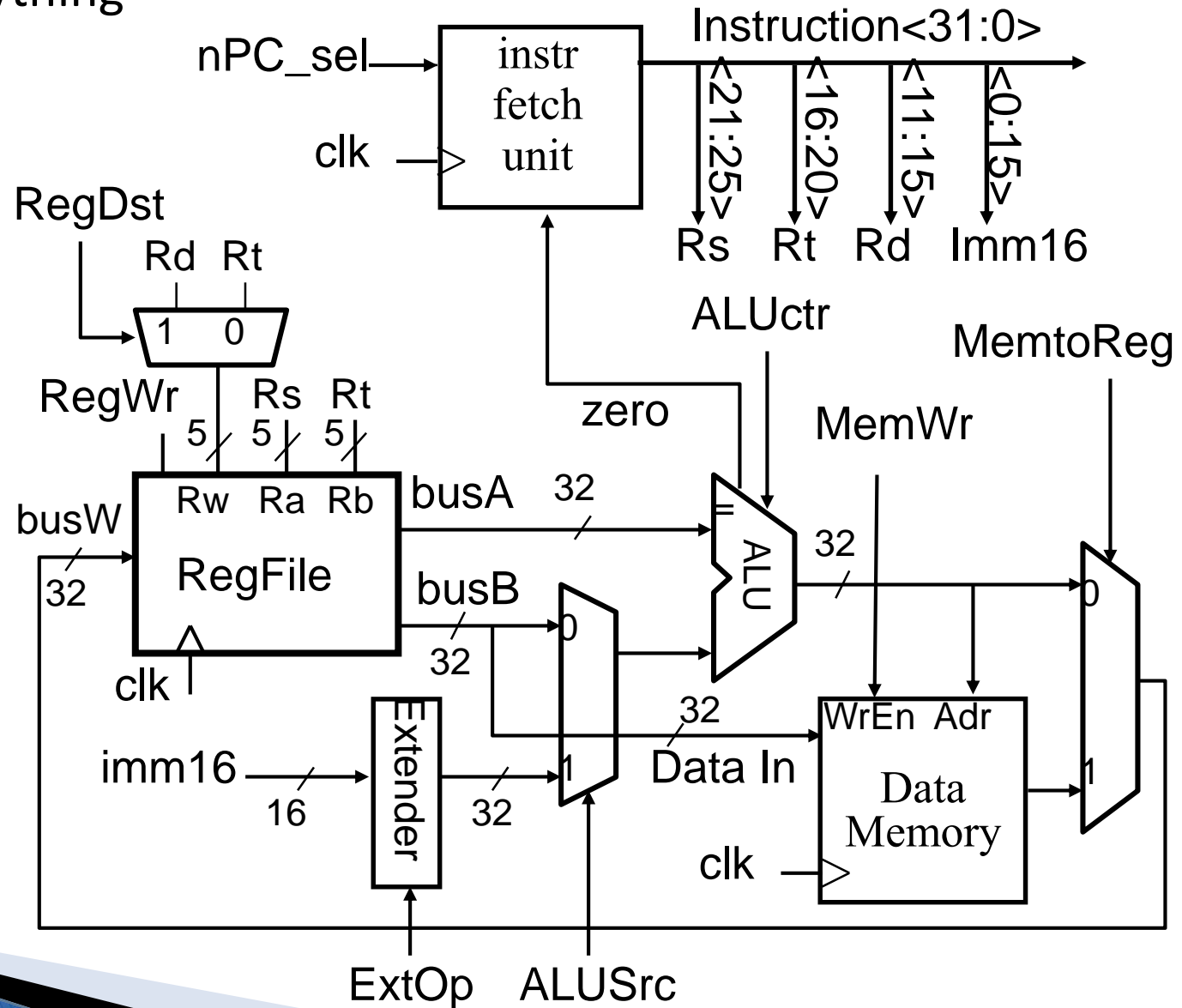
- ▶ We have everything except control signals



Meaning of the Control Signals


- ▶ nPC_sel : “+4”: $0 \Rightarrow PC \leftarrow PC + 4$
“br”: $1 \Rightarrow PC \leftarrow PC + 4 + \{SignExt(Imm16), 00\}$
“n”=next

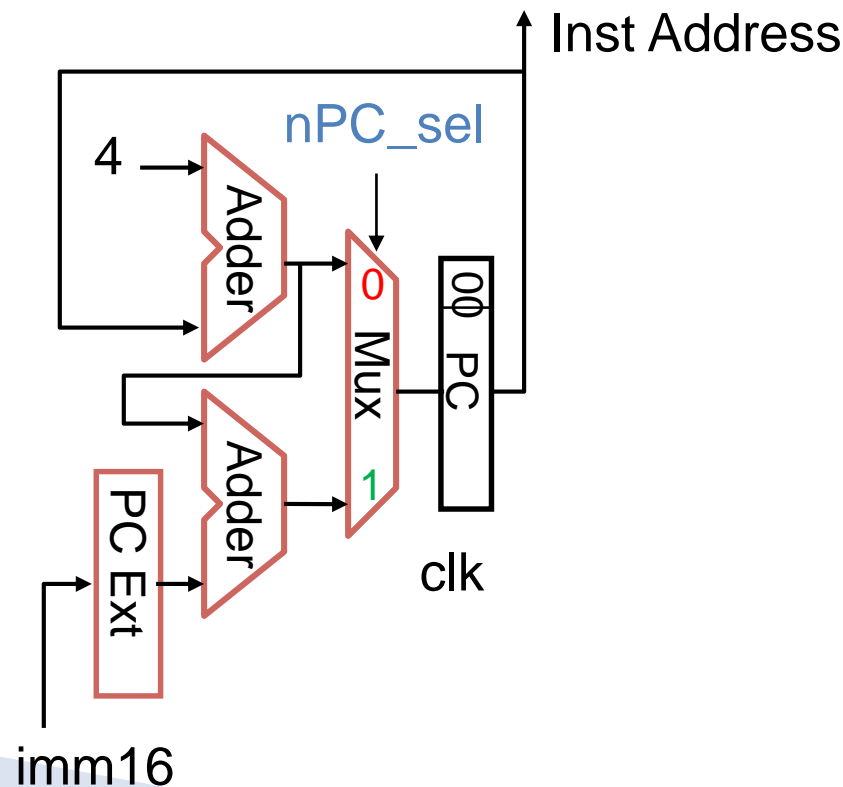- ▶ Later in lecture: higher-level connection between mux and branch condition




Meaning of the Control Signals

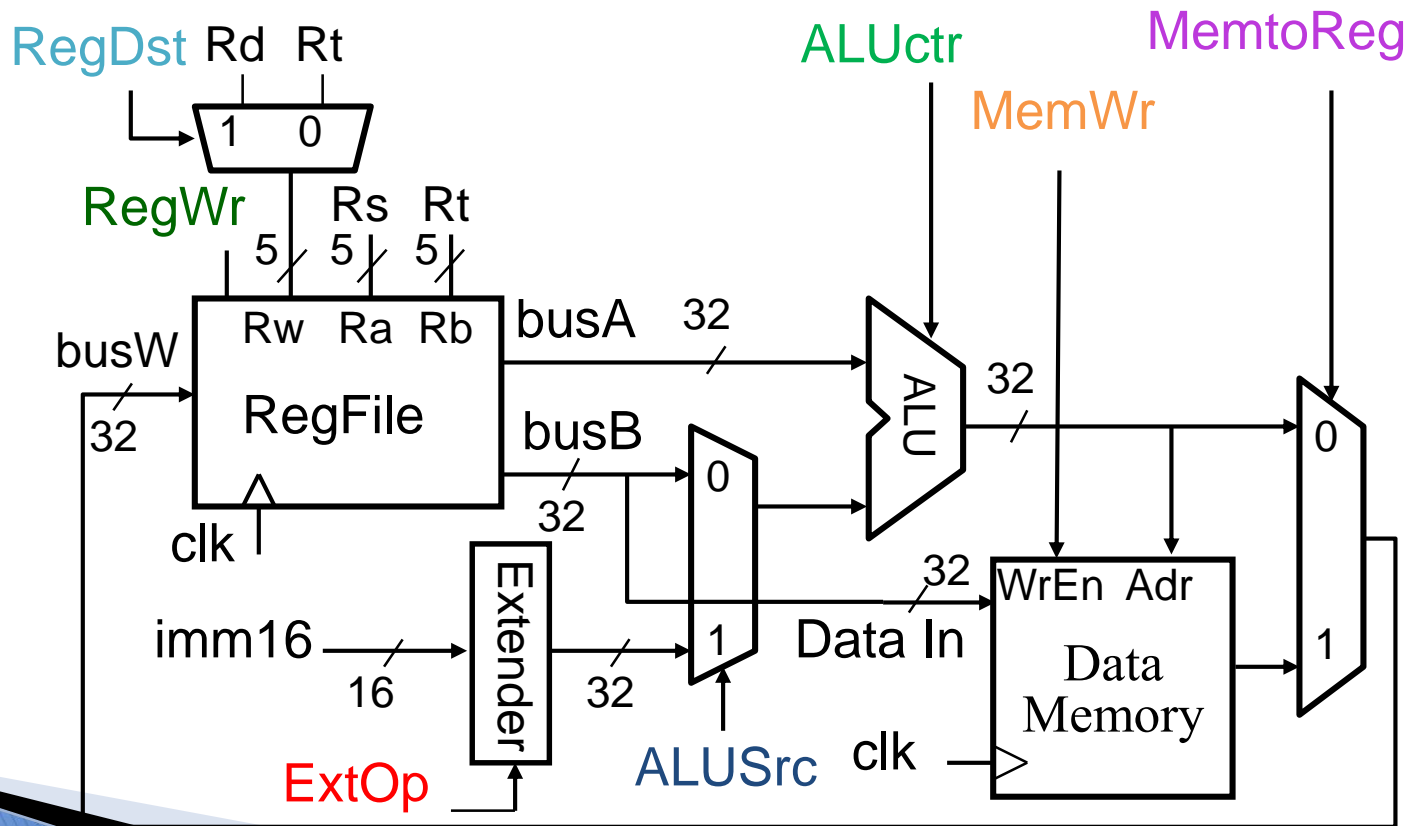- ▶ **ExtOp**: “zero”, “sign”
- ▶ **ALUsrc**: 0 \Rightarrow regB; 1 \Rightarrow immedi
- ▶ **ALUctr**: “ADD”, “SUB”, “OR”
- **MemWr**: 1 \Rightarrow write memory
- **MemtoReg**: 0 \Rightarrow ALU; 1 \Rightarrow Mem
- **RegDst**: 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- **RegWr**: 1 \Rightarrow write register



The Add Instruction

 

add rd, rs, rt


- MEM[PC] Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$ The actual operation
- $PC = PC + 4$ Calculate the next instruction's address

Instruction Fetch Unit start of Add


- Fetch the instruction from Instruction memory:

Instruction = MEM[PC]


- same for all instructions

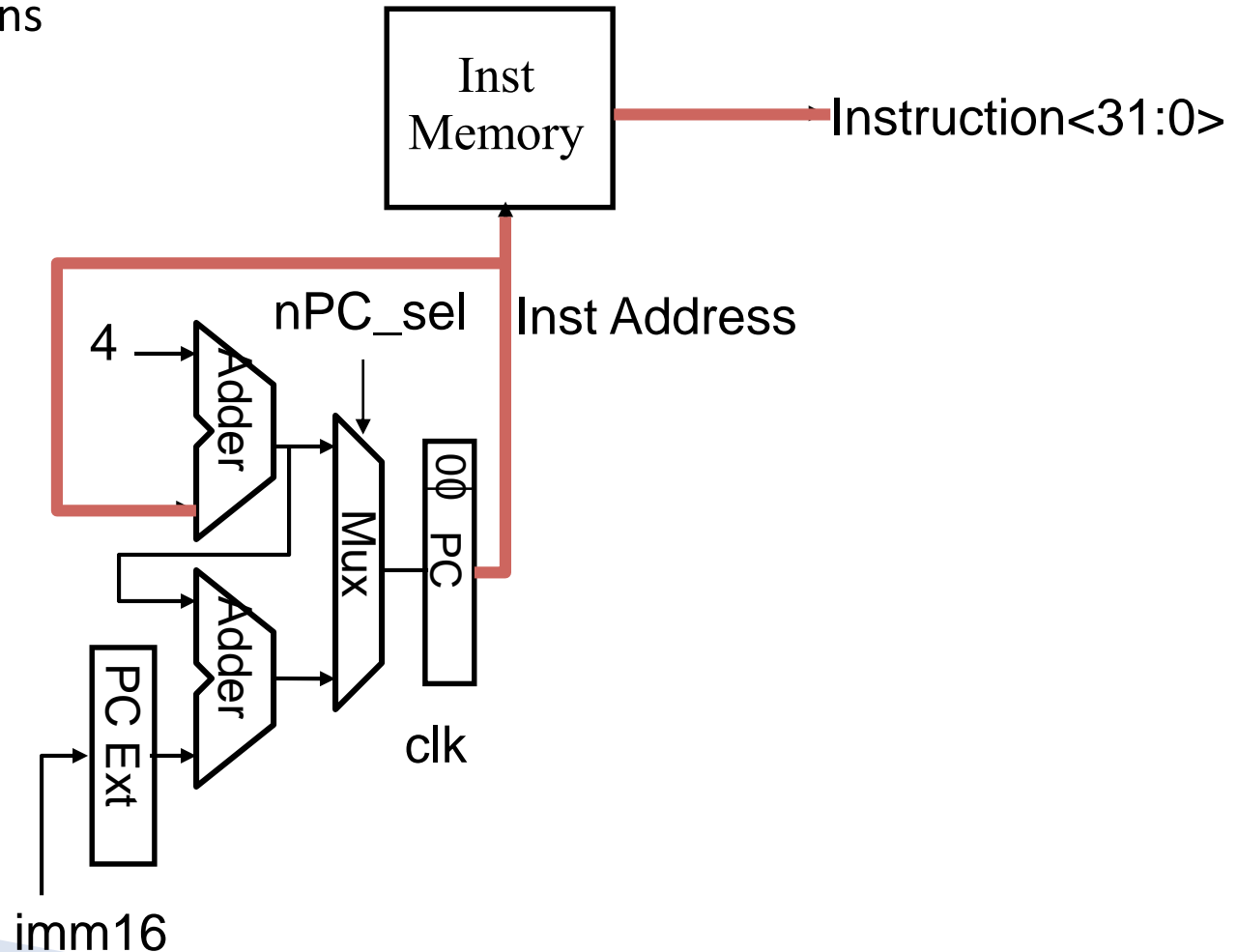

The Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

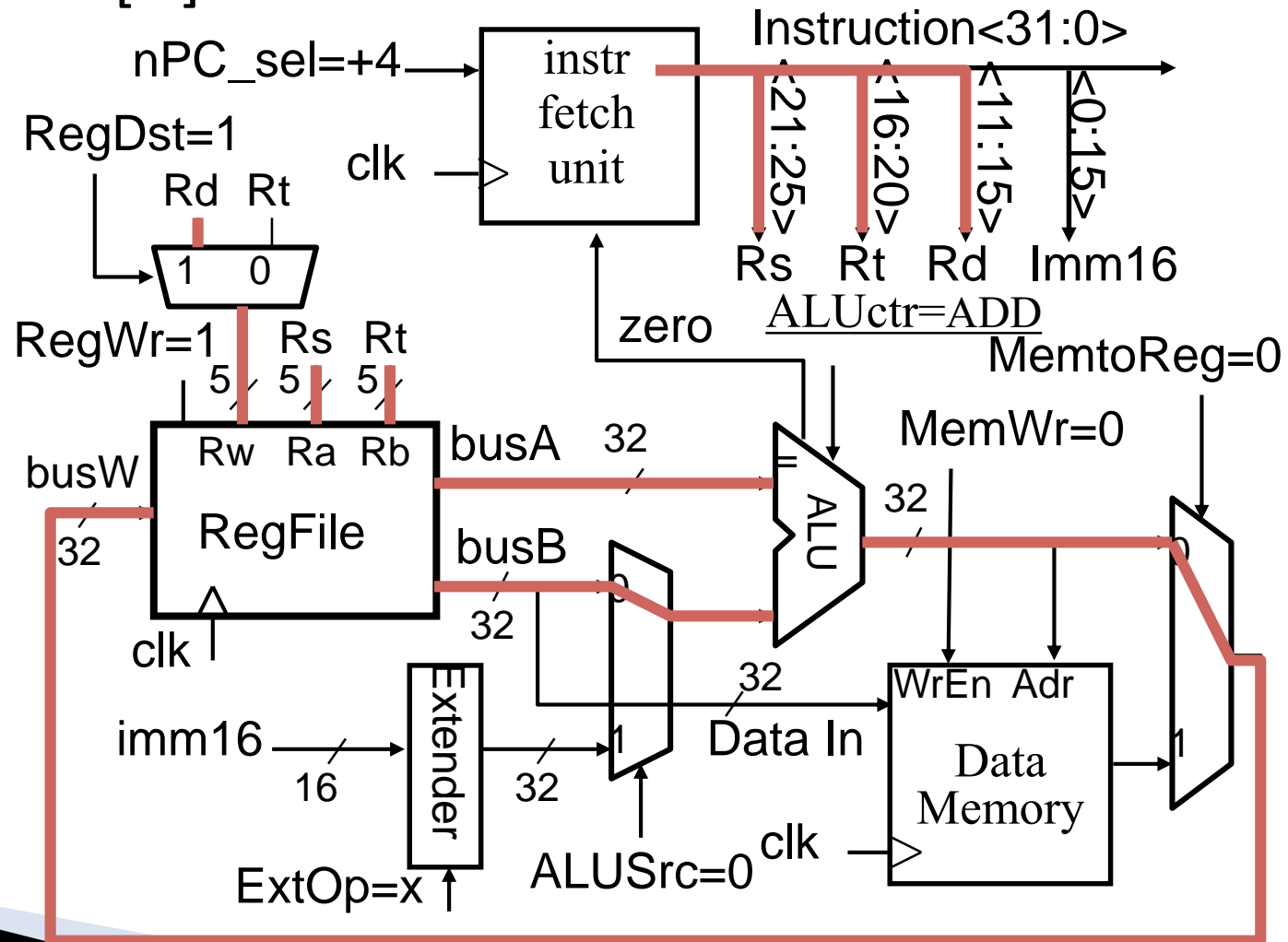


Instruction Fetch Unit end of Add

 
- ▶ $PC = PC + 4$
 - This is the same for all instructions except: Branch and Jump




Single Cycle Datapath for Ori

 

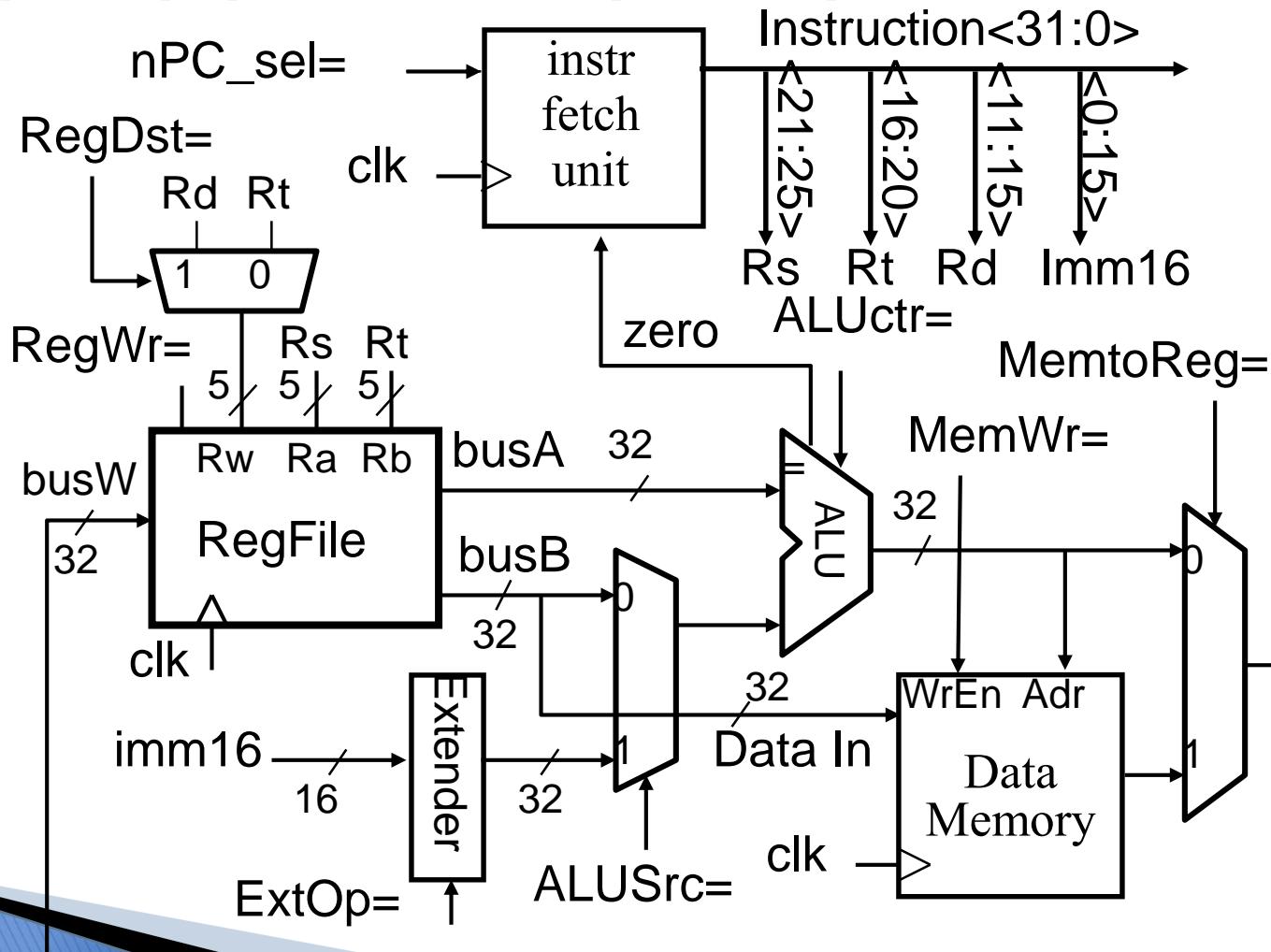
► $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




Single Cycle Datapath for Ori

 

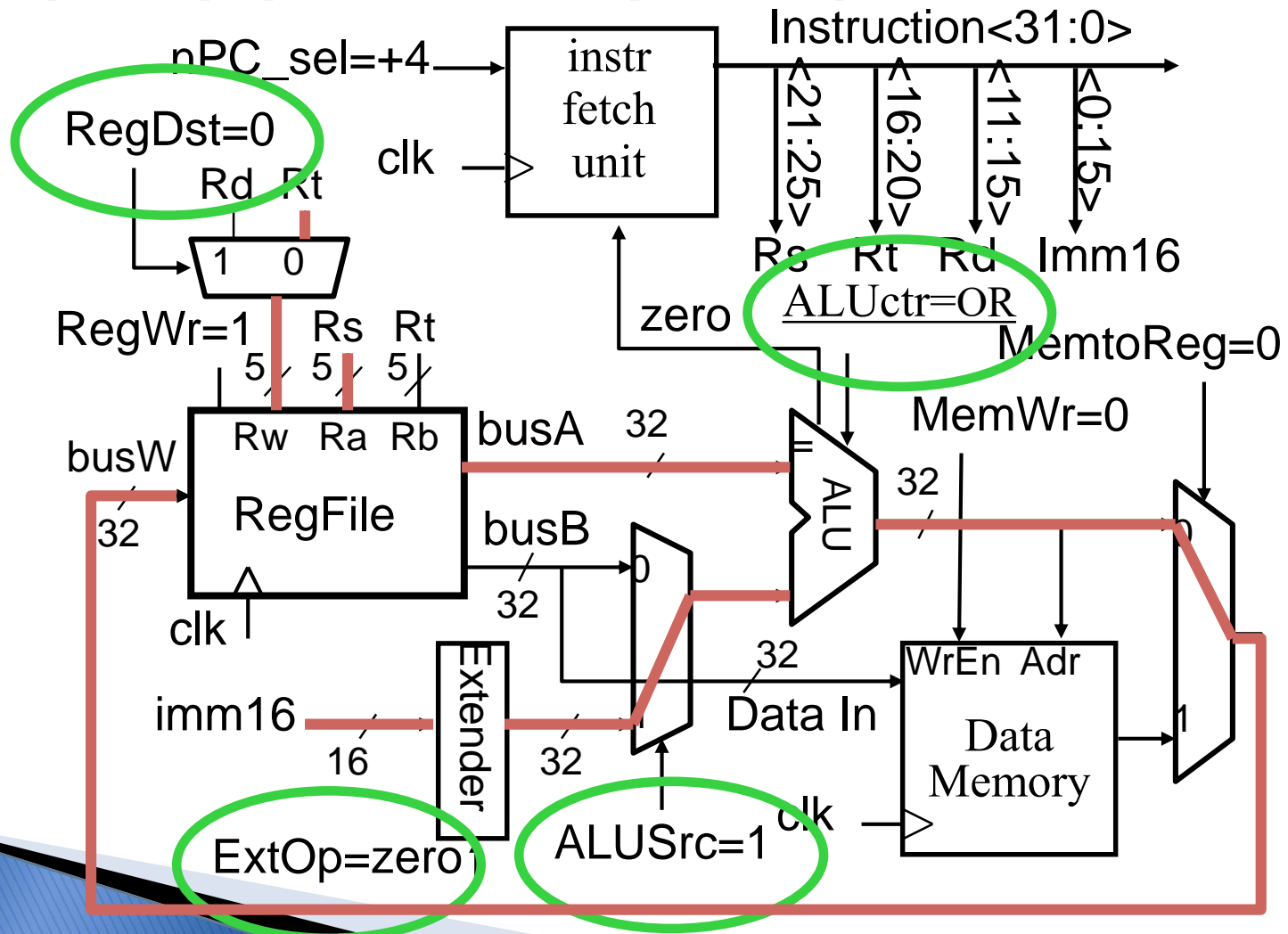
- ▶ $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




Single Cycle Datapath for LW

 

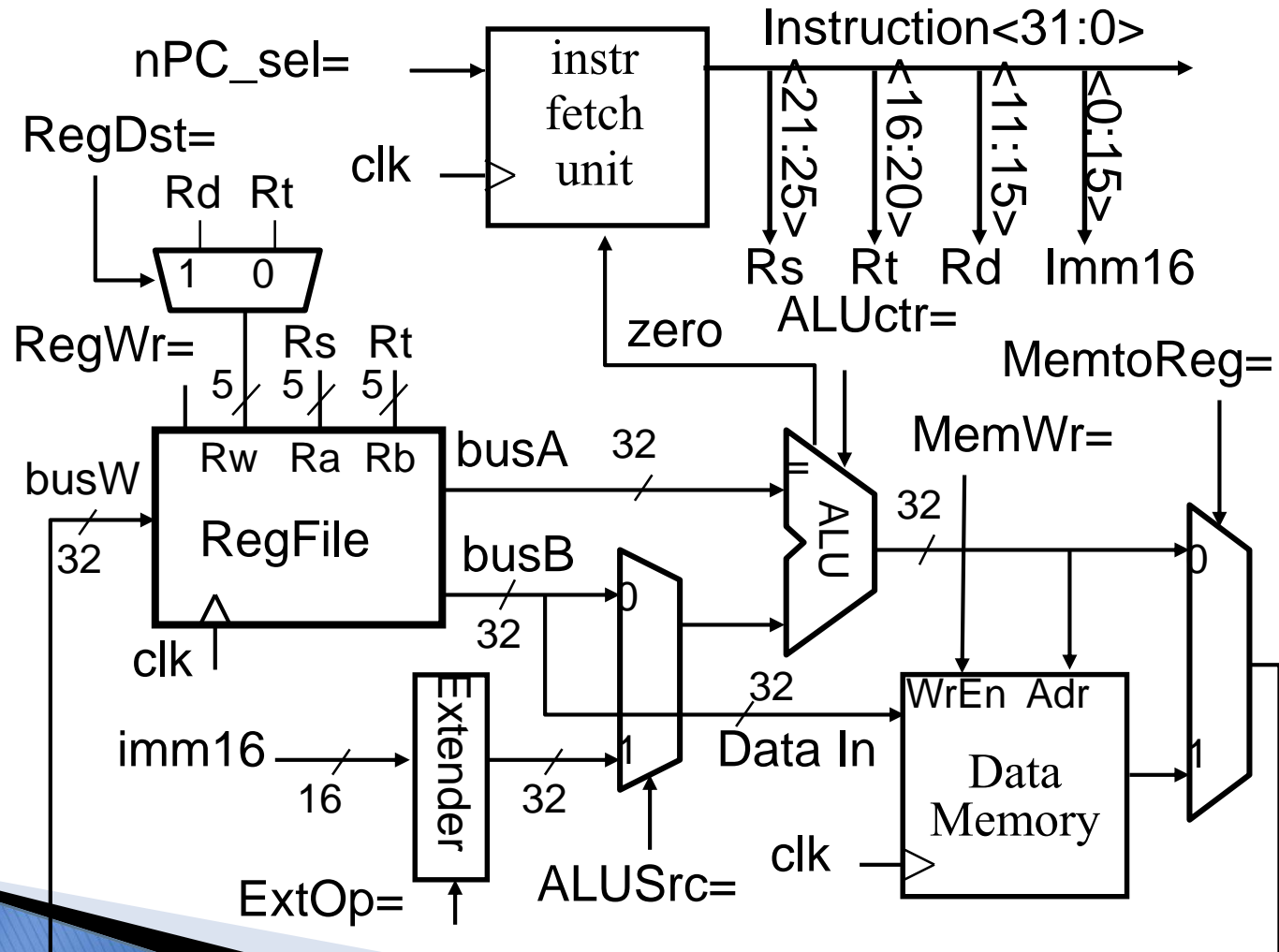
- ▶ $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




Single Cycle Datapath for LW

 

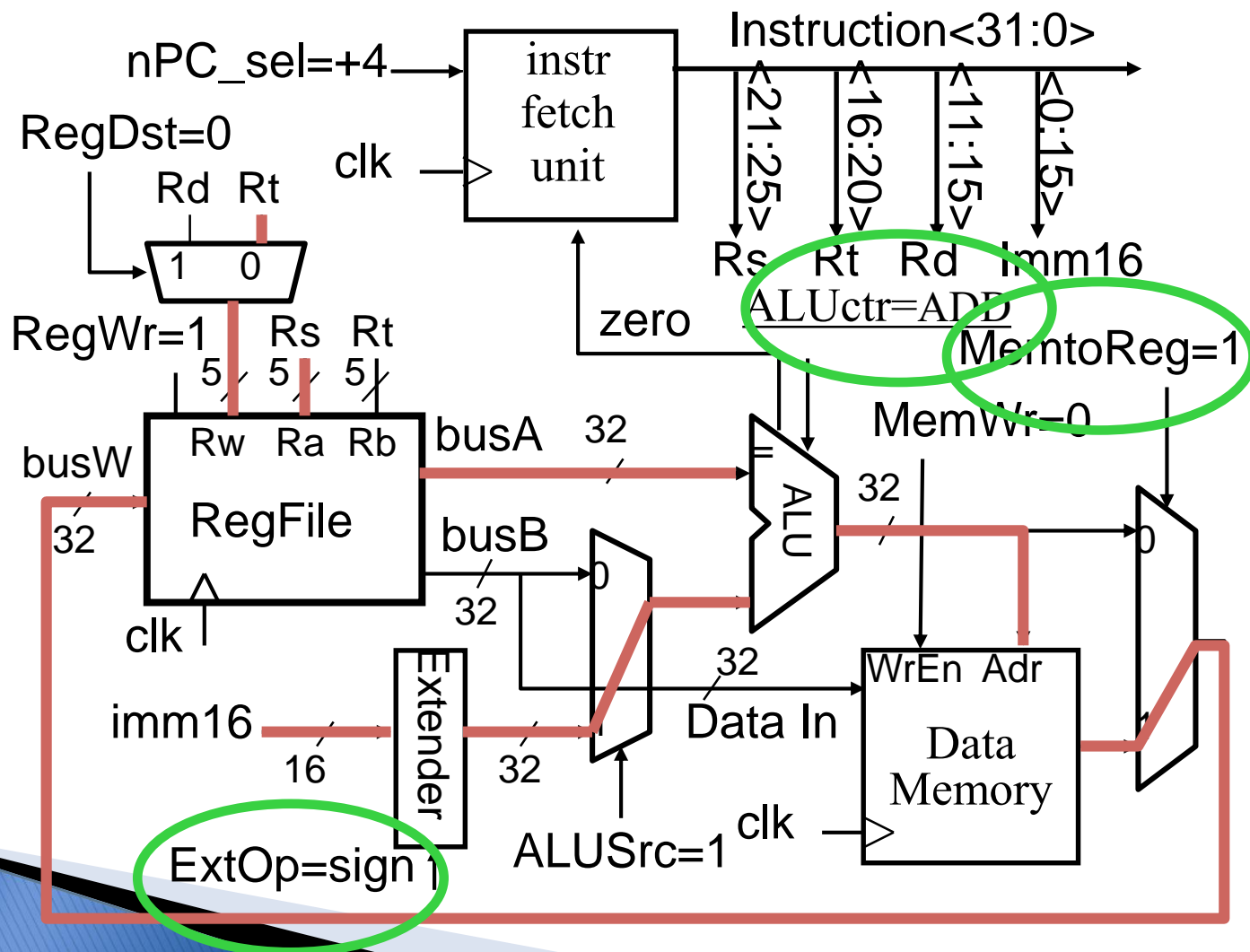
- ▶ $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




Single Cycle Datapath for SW

 

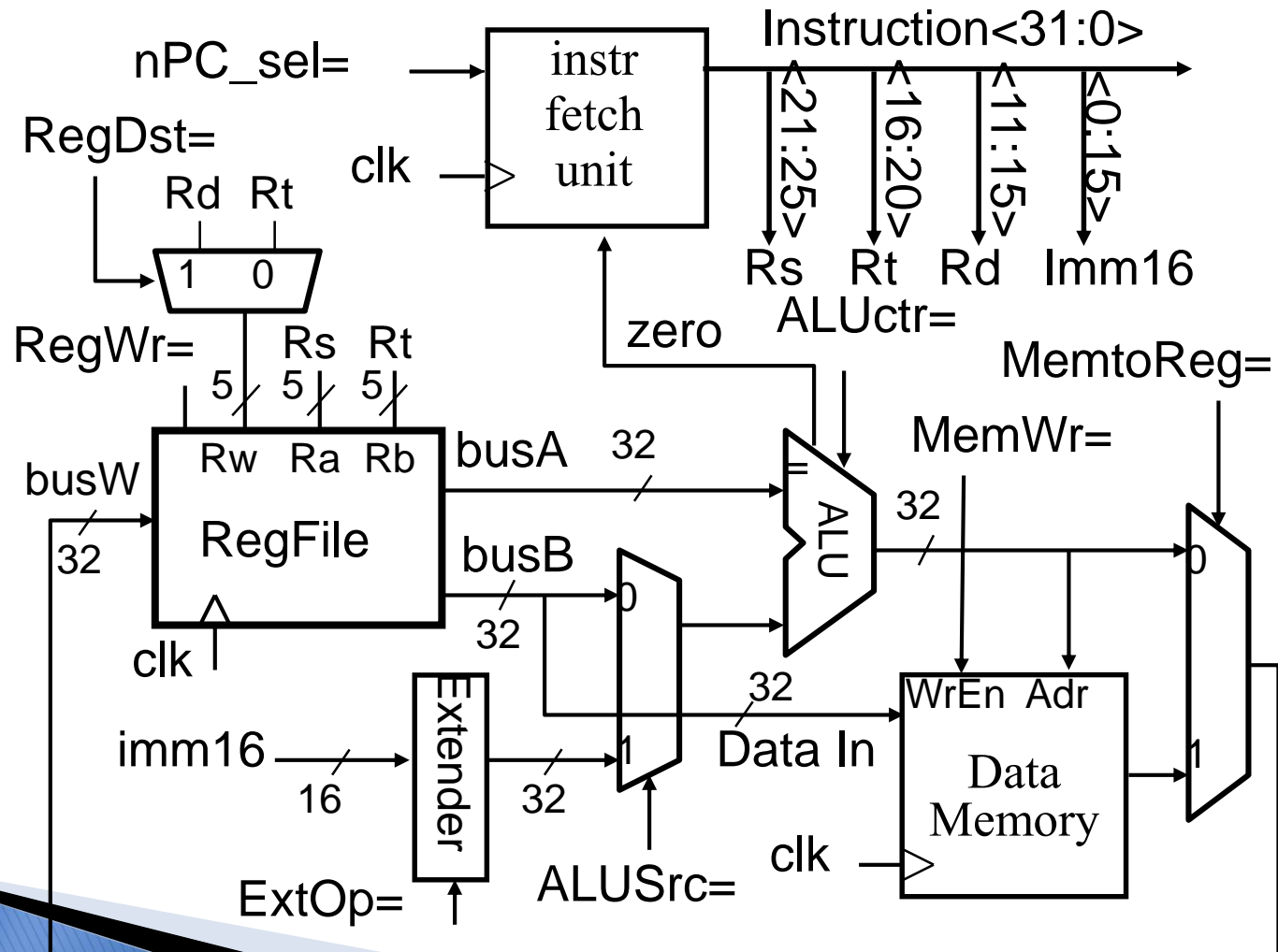- ▶ Data Memory $\{R[rs] + \text{SignExt}[\text{imm16}]\} = R[rt]$



Single Cycle Datapath for SW

 

- ▶ Data Memory $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$

